

AKTU



B. Tech I-Year

Gateway Classes



Semester -I & II

Common to All Branches

BEE101/201: FUNDAMENTALS OF ELECTRICAL ENGG.

UNIT-3 :: Transformers



Gateway Series for Engineering

- ✓ **Topic Wise Entire Syllabus**
- ✓ **Long - Short Questions Covered**
- ✓ **AKTU PYQs Covered**
- ✓ **DPP**
- ✓ **Result Oriented Content**



Download App

For Full Courses including Video Lectures

AKTU



B. Tech I-Year

Gateway Classes



BEE101 / BEE201: FUNDAMENTALS OF ELECTRICAL ENGINEERING

Unit-3

Introduction to : Transformers

Syllabus

1. Magnetic circuits, ideal and practical transformer, equivalent circuit, losses in transformers, regulation, and efficiency



Download App

For Full Courses including Video Lectures 

- **Unit-3: (Transformers)**

- Magnetic circuits, ✓
- ideal and practical transformer, ✓
- equivalent circuit, ✓
- losses in transformers, ✓
- regulation and efficiency. ✓

Gateway classes 7455 9612 84

Basic Definitions

1. **Magnetic Field**:- Area around a magnet within which its influence is perceptible is known as magnetic field

2. **Magnetic Flux** (Φ) :- total number of magnetic field lines passing through a given surface. unit of flux is Weber (Wb). $1 \text{ wb} = 10^8$ line of force

3. **Magnetic Flux density**:- Flux per unit area is known as flux


$$\text{density } (B) = \frac{\text{flux}}{\text{area}}$$

4. **Magnetic field intensity**:- Magnetizing force or Magnetic field intensity or magnetic field strength is the MMF required to magnetize a unit length of the magnetic flux path. The unit of magnetic field intensity is AT/m and is denoted by H.

$$H = \frac{NI}{l}$$

AT/m

$$H \propto I$$

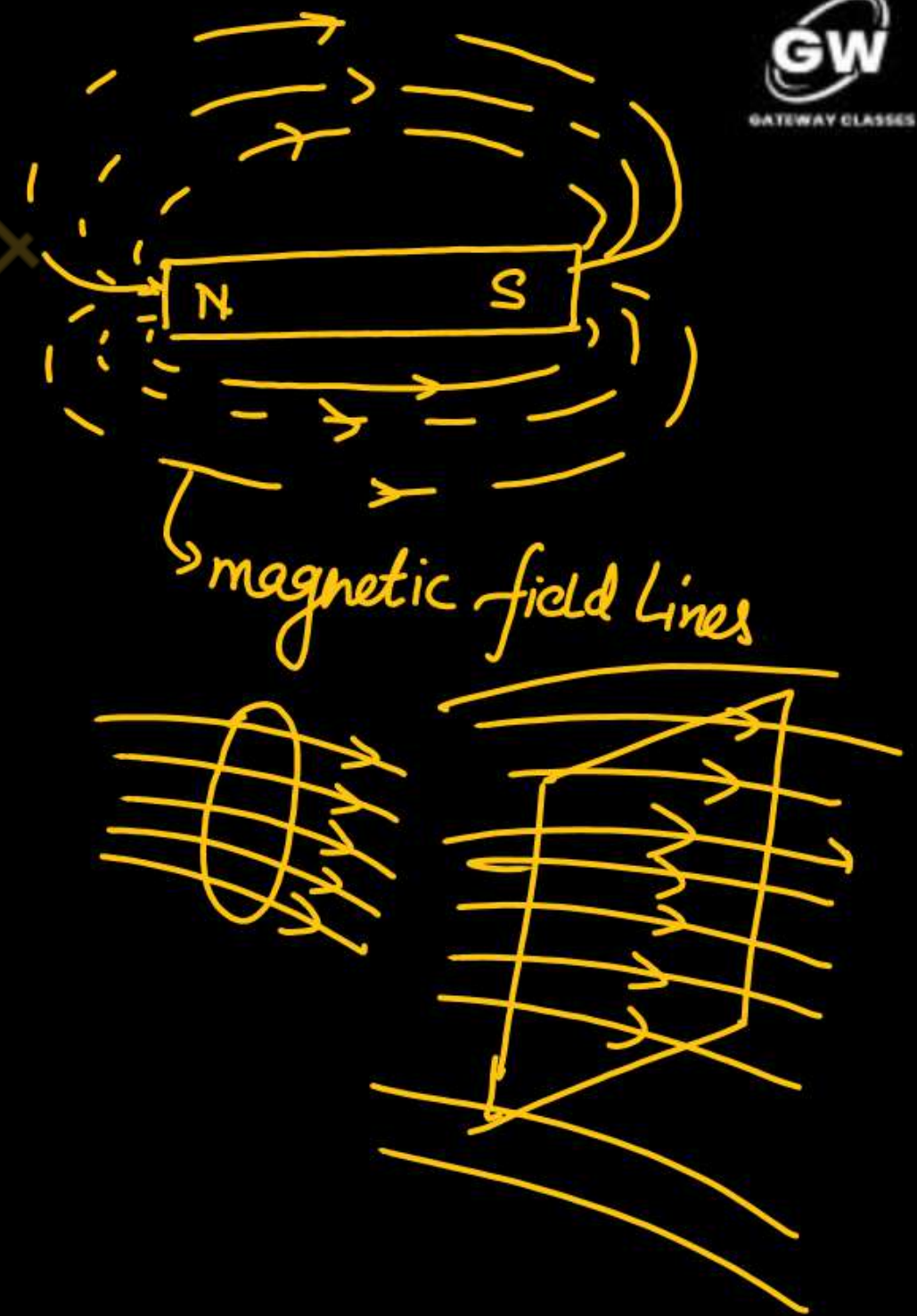

5. Magneto-motive force or MMF:- MMF is the cause for producing the magnetic flux. The MMF in a magnetic circuit depends on the number of turns(N) and the amount of current(I) flowing through it.

$$\boxed{MMF = NI}$$

unit is ampere turns. [AT]

6 Reluctance:- It is the opposition that the magnetic circuit offers for the flow of magnetic flux. We can also define the reluctance as the ratio of magneto-motive force to the magnetic flux. It is denoted by S and its unit is ampere-turns per weber.

$$Reluctance(S) = \frac{mmf}{Flux} = \frac{l}{A\mu_0\mu_r} = \frac{l}{\mu_0\mu_r A}$$

$\mu_r = \mu_0\mu_r$

$$R = \frac{\mathcal{E}^{mf}}{I} = \int \frac{dl}{a}$$

7. Permeance:- Permeance is the reciprocal of reluctance. The ease with which the flux can pass through the material is known as permeance. Weber/AT is the unit of permeance.

8. Permeability:- Permeability is the ability of a material to allow the magnetic flux when the object is placed inside the magnetic field.

$$\boxed{\mu = \mu_0\mu_r}$$

Where μ_0 is absolute permeability ($4\pi \times 10^{-7}$) and $\mu_r = 1$ for air is relative permeability

Magnetic Circuit:- The closed path followed by the magnetic flux is magnetic circuit.

The laws of magnetic circuits are quite similar to the electric circuits.

A **magnetic circuit** is made up of magnetic materials having high permeability such as iron, soft steel, etc. Consider a solenoid having N turns wound on an iron core. The magnetic flux of ϕ Weber sets up in the core when the current of I ampere is passed through a solenoid.

Let, l = mean length of the magnetic circuit, A = cross-sectional area of the core

μ_r = relative permeability of the core

Now the Field Strength is given by

$$H = \frac{NI}{l} \quad \text{AT/m}$$


$$B = \mu_0 \mu_r H = \frac{\mu_0 \mu_r NI}{l} \quad \text{Wb/m}^2 \quad \text{Wb}$$

$$\text{Total Flux } \phi = B \times A = \frac{\mu_0 \mu_r NIA}{l} = \frac{NI}{\frac{l}{A\mu_0\mu_r}} \quad \text{Wb.}$$

The denominator $\frac{l}{A\mu_0\mu_r}$ is called reluctance of the circuit and NI is called mmf.

$$\phi = \frac{\text{mmf}}{\text{reluctance}} \quad \text{Wb}$$

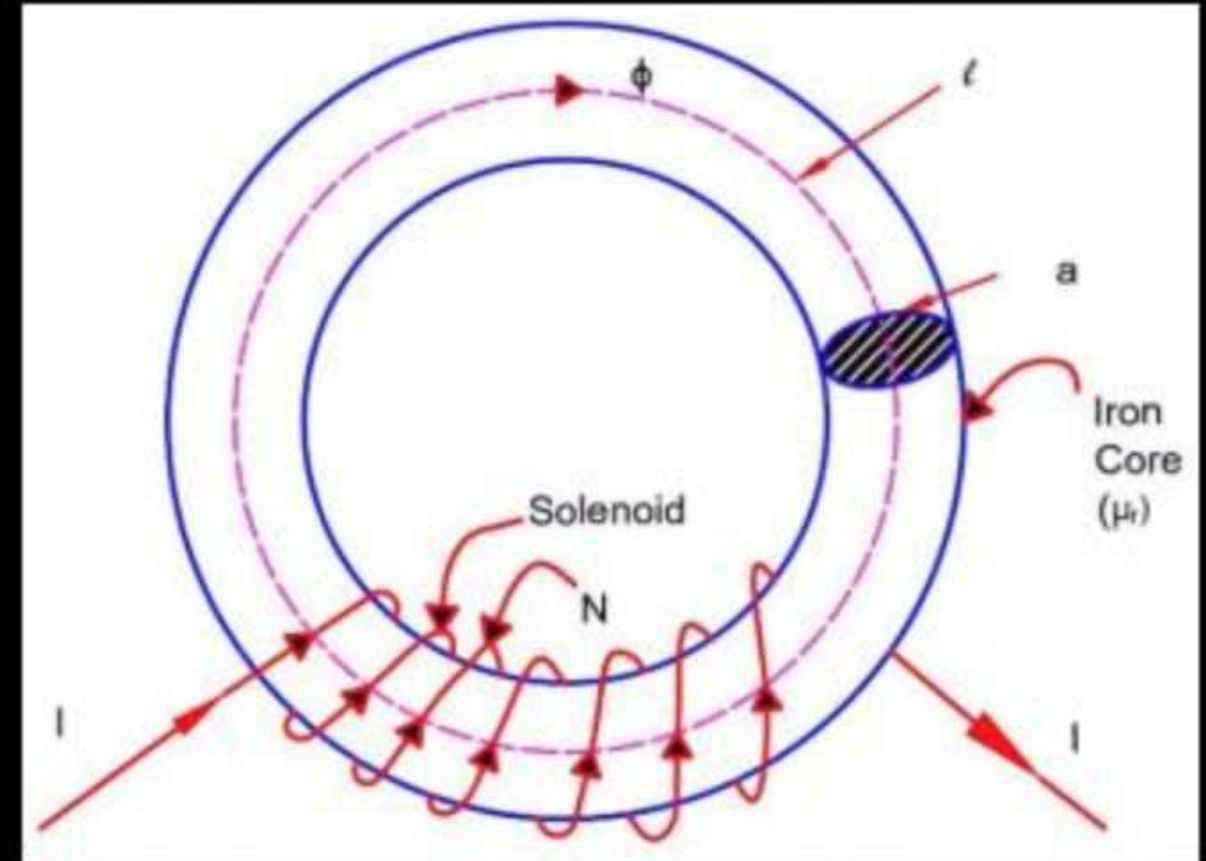this relation is similar to electric circuit $I = V/R$



Magnetic Circuit:- The closed path followed by the magnetic flux is magnetic circuit.

The laws of magnetic circuits are quite similar to the electric circuits.

A **magnetic circuit** is made up of magnetic materials having high permeability such as iron, soft steel, etc. Consider a solenoid having N turns wound on an iron core. The magnetic flux of ϕ Weber sets up in the core when the current of I ampere is passed through a solenoid.

Let, l = mean length of the magnetic circuit, A = cross-sectional area of the core

μ_r = relative permeability of the core

Now the Field Strength is given by

$$H = \frac{NI}{l} \quad \text{AT/m}$$

$$B = \mu_0 \mu_r H = \frac{\mu_0 \mu_r NI}{l} \quad \text{Wb/m}^2 \quad \text{Wb}$$

$$\text{Total Flux } \phi = B \times A = \frac{\mu_0 \mu_r NIA}{l} = \frac{NI}{\frac{l}{A\mu_0\mu_r}} \quad \text{Wb.}$$


$\rightarrow$ mmf.
 $\rightarrow$ Reluctance

The denominator $\frac{l}{A\mu_0\mu_r}$ is called reluctance of the circuit

and NI is called mmf.

$$\phi = \frac{\text{mmf}}{\text{reluctance}} \quad \text{Wb}$$

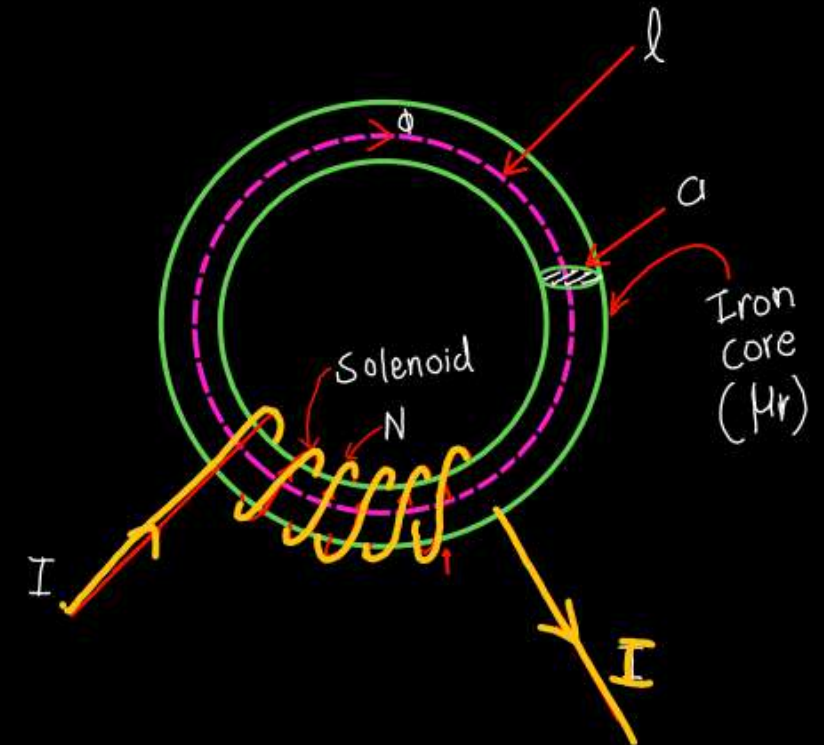this relation is similar to electric circuit $I = V/R$



Similarities

1. The closed path for magnetic flux is called a magnetic circuit.

2. Flux, $\phi = \frac{\text{m.m.f.}}{\text{reluctance}}$

3. m.m.f. (ampere-turns)

4. Reluctance, $S = \frac{l}{\mu_0 \mu_r}$

5. Flux density, $B = \frac{\phi}{a} \text{ Wb/m}^2$


6. m.m.f. drop = ϕS

7. Magnetic intensity, $H = N I / l$

8. Permeance

9. Permeability

Magnetic Circuit

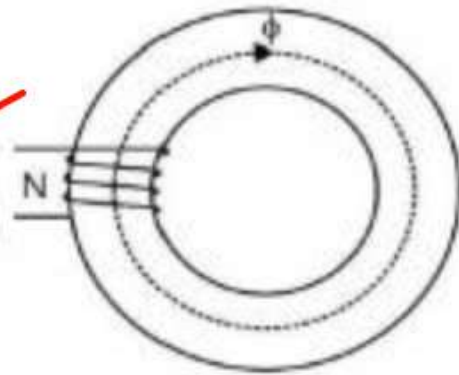

1. The closed path for electric current is called an electric circuit.

2. Current, $I = \frac{\text{e.m.f.}}{\text{resistance}}$

3. e.m.f. (volts)

4. Resistance, $R = \rho \frac{l}{a}$

5. Current density, $J = \frac{I}{a} \text{ A/m}^2$


6. Voltage drop = $I R$

7. Electric intensity, $E = V / d$

8. Conductance.

9. Conductivity

Electric Circuit

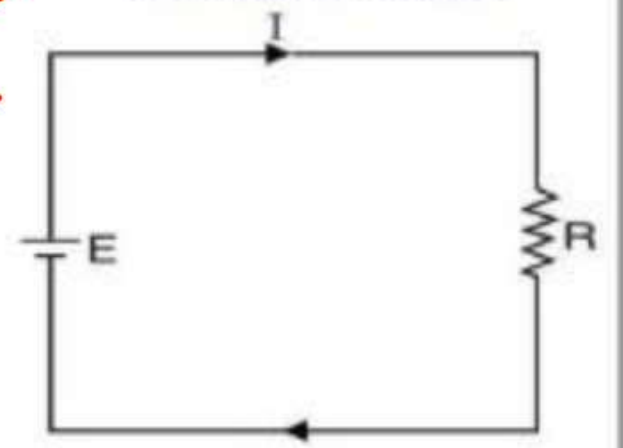

Disimilarities between Magnetic Circuit & Electric Circuit

⑤ flux can be setup through air gap

Dissimilarities

current cannot flow through air gap

- ✓ 1. Truly speaking, magnetic flux does not flow.
- ✓ 2. There is no magnetic insulator. For example, flux can be set up even in air (the best known magnetic insulator) with reasonable m.m.f.
- ✓ 3. The value of μ_r is not constant for a given magnetic material. It varies considerably with flux density (B) in the material. This implies that reluctance of a magnetic circuit is not constant rather it depends upon B .
4. No energy is expended in a magnetic circuit. In other words, energy is required in creating the flux, and not in maintaining it.

- ✓ 1. The electric current actually flows in an electric circuit.
- ✓ 2. There are a number of electric insulators. For instance, air is a very good insulator and current cannot pass through it.
3. The value of resistivity (ρ) varies very slightly with temperature. Therefore, the resistance of an electric circuit is practically constant. This salient feature calls for different approach to the solution of magnetic and electric circuits.
4. When current flows through an electric circuit, energy is expended so long as the current flows. The expended energy is dissipated in the form of heat.

Series Magnetic Circuit

- Series magnetic circuits** :- consider a circular ring made from different materials of lengths l_1, l_2 and l_3 , cross-sectional areas a_1, a_2 and a_3 and relative permeability μ_{r1}, μ_{r2} and μ_{r3} respectively with a cut of length l_g called air gap. The total reluctance is the arithmetic sum of individual reluctance as they are joined in series.

$$S_A = \frac{l_1}{\mu_0 \mu_{r1} a_1}, S_2 = \frac{l_2}{\mu_0 \mu_{r2} a_2}, S_3 = \frac{l_3}{\mu_0 \mu_{r3} a_3}$$


$$S_g = \frac{l_g}{\mu_0 a_g}$$

$$S = S_A + S_B + S_C + S_g$$

$$S = \frac{l_1}{\mu_0 \mu_{r1} a_1} + \frac{l_2}{\mu_0 \mu_{r2} a_2} + \frac{l_3}{\mu_0 \mu_{r3} a_3} + \frac{l_g}{\mu_0 a_g}$$

$$\text{mmf} = \phi \times S$$
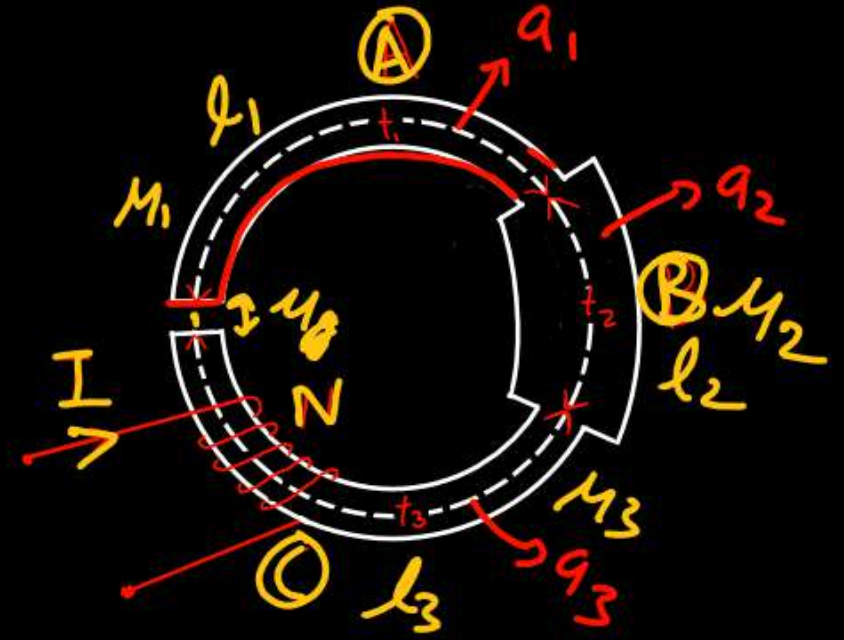
$$S = \underbrace{\phi \frac{l_1}{\mu_0 \mu_{r1} a_1}}_{\text{mmf}_1} + \underbrace{\phi \frac{l_2}{\mu_0 \mu_{r2} a_2}}_{\text{mmf}_2} + \underbrace{\frac{l_3}{\mu_0 \mu_{r3} a_3} \times \phi}_{\text{mmf}_3} + \underbrace{\frac{l_g}{\mu_0 a_g} \times \phi}_{\text{mmf}_g}$$




Parallel Magnetic Circuit

A magnetic circuit which has more one path for the magnetic flux is called as **parallel magnetic circuit**.

Consider a coil of N turns wound on limb BD carries an electric current of I amperes. The magnetic flux ϕ set up by the coil divides at B into two paths. The magnetic flux ϕ_2 passes along the path BCD. The magnetic flux ϕ_1 passes along the path BAD.

Therefore, the total flux is,

$$\Phi = \phi_1 + \phi_2$$

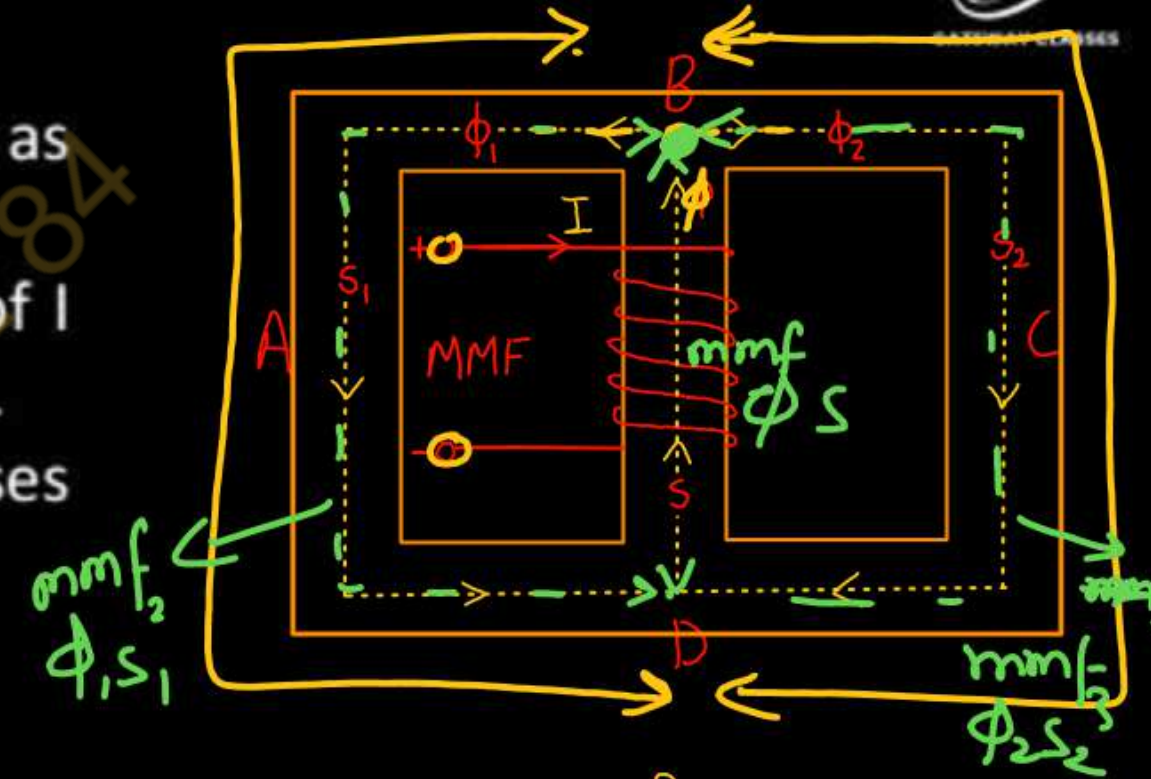

The path BD and BCD are in parallel and hence form a parallel magnetic circuit. In a parallel magnetic circuit, the MMF required for the whole parallel magnetic circuit is equal to MMF required for any one of the parallel paths.

Let


S = Reluctance of magnetic path BD, S_1 = Reluctance of magnetic path BAD

S_2 = Reluctance of magnetic path BCD

Therefore,

Total MMF = MMF for path ABD + MMF for path BD or BCD
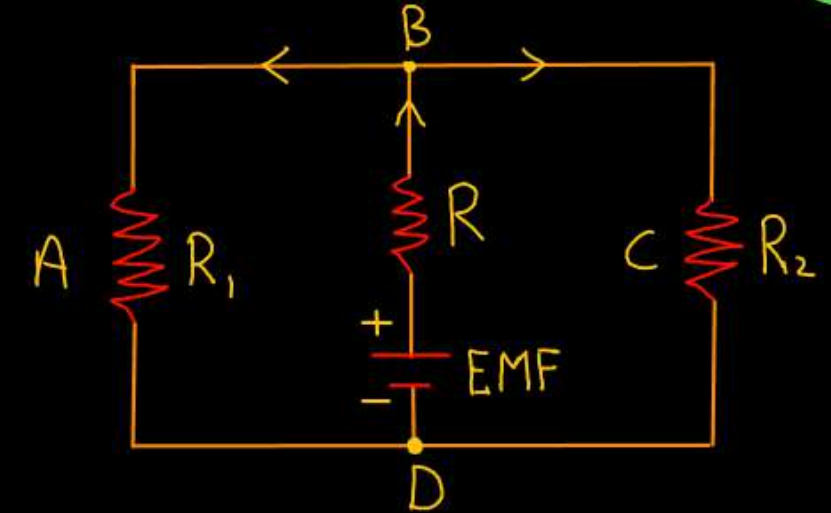
$$\text{MMF} = \phi \cdot S + \phi_2 \cdot S_2 = \phi \cdot S + \phi_1 \cdot S_1$$



Leakage Flux:- The part of magnetic flux that does not follow the desired path in a magnetic circuit is known as *leakage flux*.

Flux can be divided into two main components

- magnetic flux throughout the magnetic circuit including air gap is known as **useful flux (ϕ_g)**
- leakage flux** Link partially with magnetic circuit and complete its path through air.


Leakage Flux = Total flux - useful flux

$$\phi_{\text{leakage}} = \phi_i - \phi_g$$

Leakage Coefficient, $\lambda = \frac{\text{Total Magnetic Flux } (\phi_i)}{\text{Useful Magnetic Flux } (\phi_g)}$

Magnetic Fringing:- When the magnetic field lines pass through an air gap, they tend to bulge out. It is because the magnetic field lines repel each other when passing through the air. This effect is known as *magnetic fringing*.

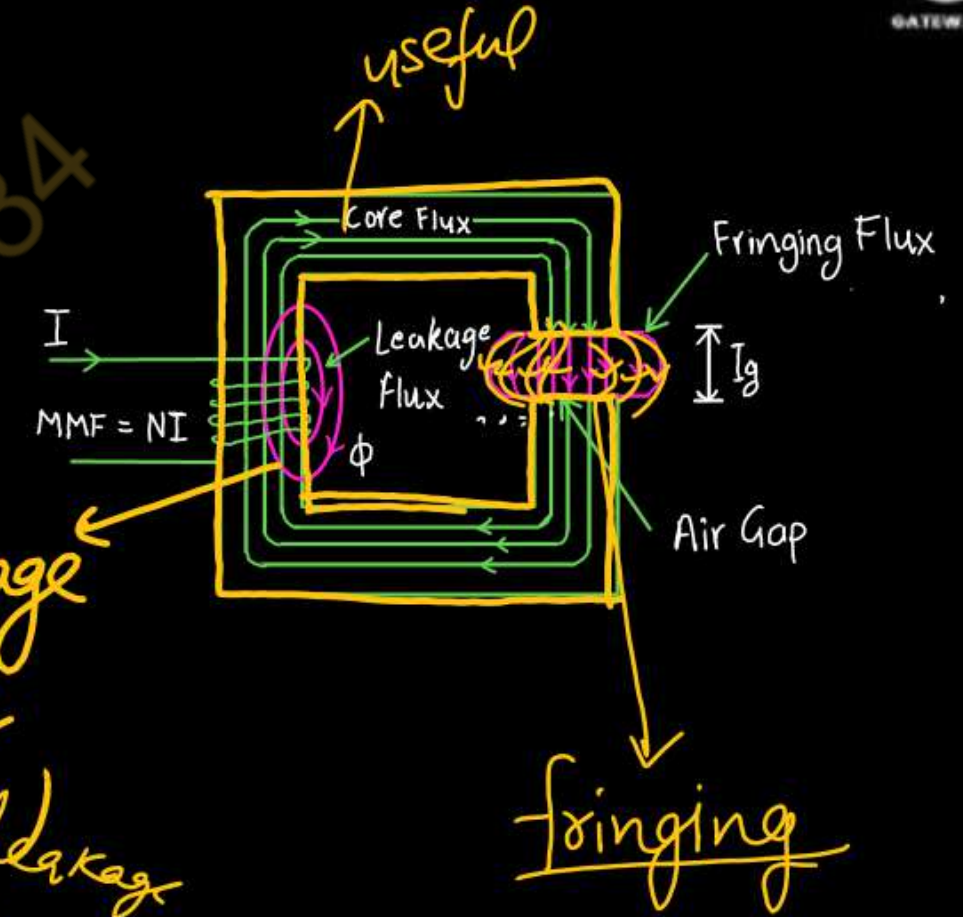Due to magnetic fringing, the effective area of the air gap is increased and thus the magnetic flux density is decreased in the air gap. The longer the air gap, the higher is the fringing and *vice-versa*.



$$\phi_i = \phi_{\text{useful}} + \phi_{\text{leakage}}$$

Transformers

Unit-3 | Lec-2

Today's Target

- ✓ Concept of Electromagnetic Induction
- ✓ Construction & Working of Transformer
- ✓ Ideal & Practical Transformer
- ✓ Transformer on Load and No Load

Faraday's law of Electromagnetic Induction

First law: Whenever a conductor is placed in a varying magnetic field, EMF induces and this emf is called an induced emf and if the conductor is a closed circuit than the induced current flows through it.

Second law: The magnitude of the induced EMF is equal to the rate of change of flux linkages.


$$e = N \frac{d\phi}{dt}$$

Based on his experiments we now have Faraday's law of electromagnetic induction according to which the amount of voltage induced in a coil is proportional to the number of turns and the changing magnetic field of the coil.

So now, the induced voltage is as follows:

$$e = N \times d\Phi / dt$$

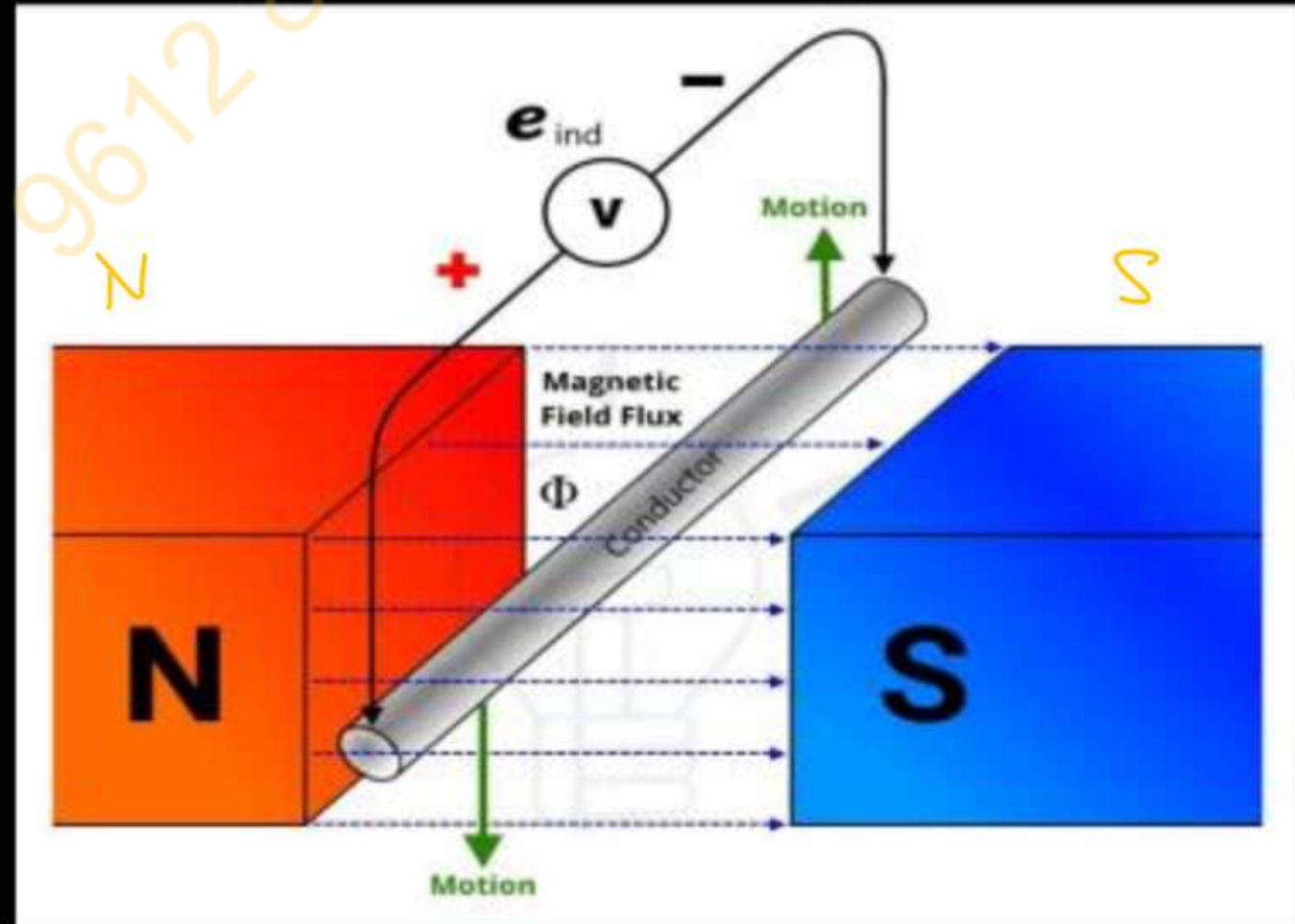Faraday's Laws of Electromagnetic Induction



Self-inductance :- It is defined as the property of the coil due to which it opposes the change of current flowing through it. Inductance is attained by a coil due to the self-induced emf produced in the coil itself by changing the current flowing through it.

If the current in the coil is increasing, the self-induced emf produced in the coil will oppose the rise of current, that means the direction of the induced emf is opposite to the applied voltage.

$$e = L \frac{dI}{dt}$$



$$L = \frac{e}{dI/dt}$$

Mutual Inductance between the two coils is defined as the property of the coil due to which it opposes the change of current in the other coil, or you can say in the neighboring coil.

When the current in the neighboring coil changes, the flux sets up in the coil and because of this, changing flux emf is induced in the coil called Mutually Induced emf and the phenomenon is known as **Mutual Inductance**.

$$e_m = M \frac{dI_1}{dt}$$
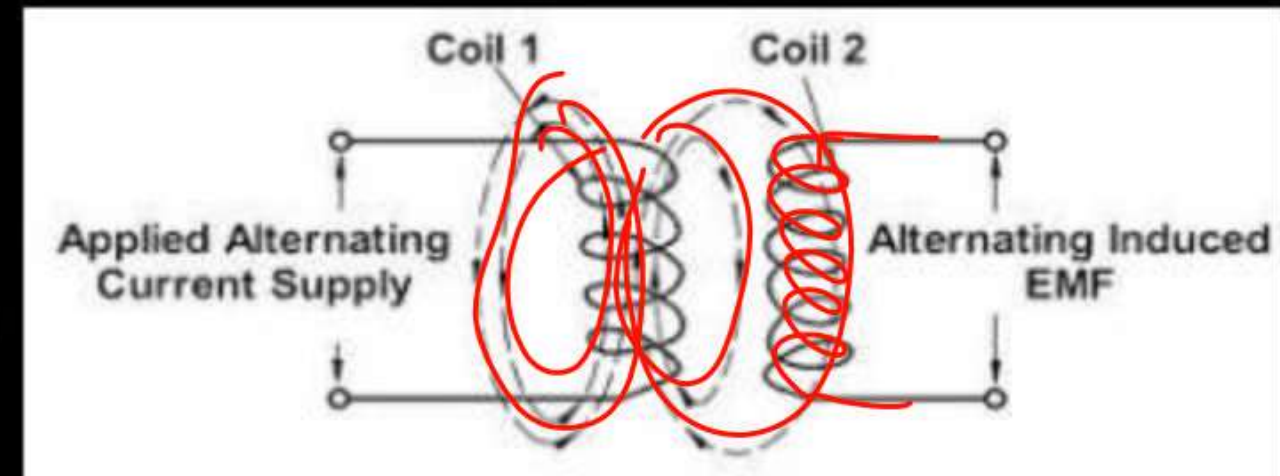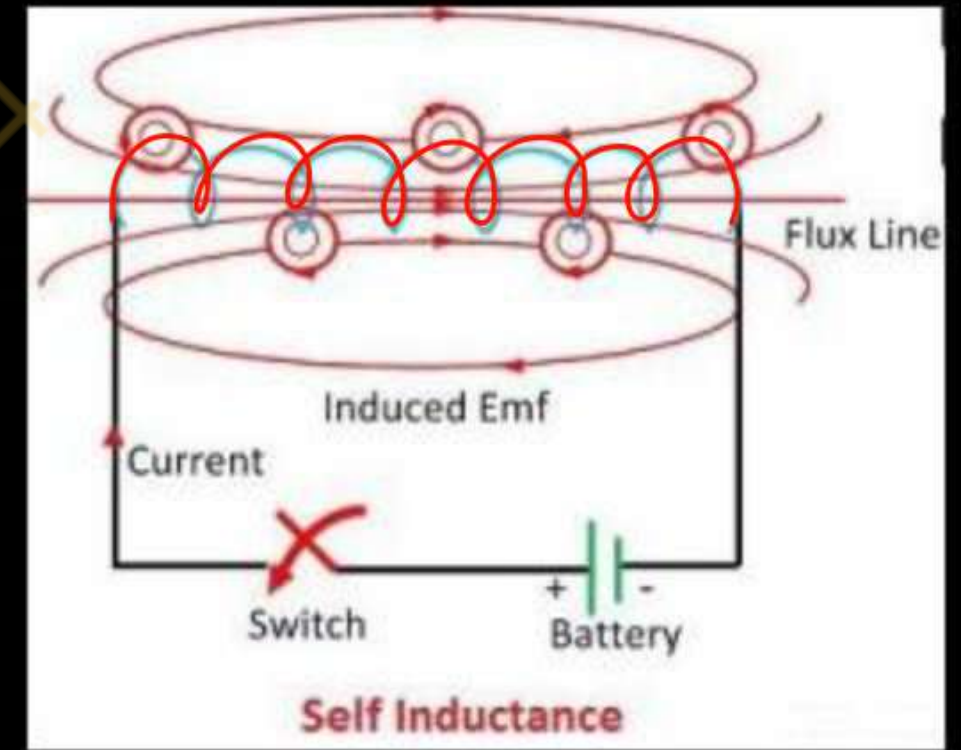
$$M = \frac{e_m}{dI_1/dt} \dots\dots\dots(1)$$




A transformer is a static electrical machine which is used for either increasing or decreasing the voltage level of the AC supply with a corresponding decrease or increase in the current at constant frequency.

Working Principle of Transformer

$$V_1 I_1 = V_2 I_2$$

$$Power = Constant$$

- The **basic principle behind working of a transformer** is the phenomenon of mutual induction between two windings linked by common magnetic flux.
- Transformer consists of two inductive coils; primary winding and secondary winding.
- When, primary winding is connected to a source of alternating voltage, alternating magnetic flux is produced around the winding.
- The core provides magnetic path for the flux, to get linked with the secondary winding.
- As the flux produced is alternating, EMF gets induced in the secondary winding according to Faraday's law of electromagnetic induction.
- This emf is called 'mutually induced emf', and the frequency of mutually induced emf is same as that of supplied emf.
- If the secondary winding is closed circuit, then mutually induced current flows through it, and hence the electrical energy is transferred from one circuit (primary) to another circuit (secondary).

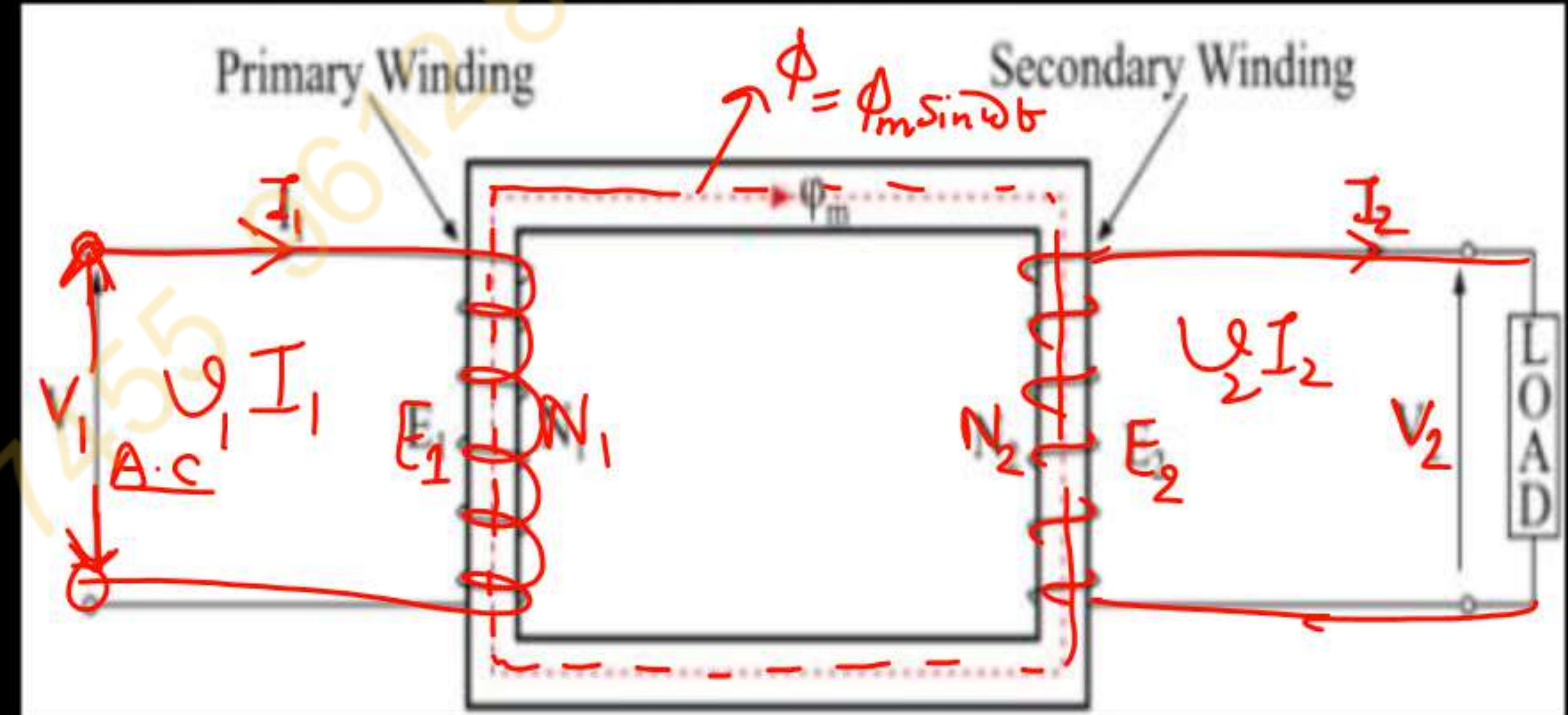

Transformer (Turns Ratio)

$$E_1 = -N_1 d\phi_m / dt$$


and

$$E_2 = -N_2 d\phi_m / dt$$

Therefore

$$E_2 / E_1 = N_2 / N_1 \approx K$$
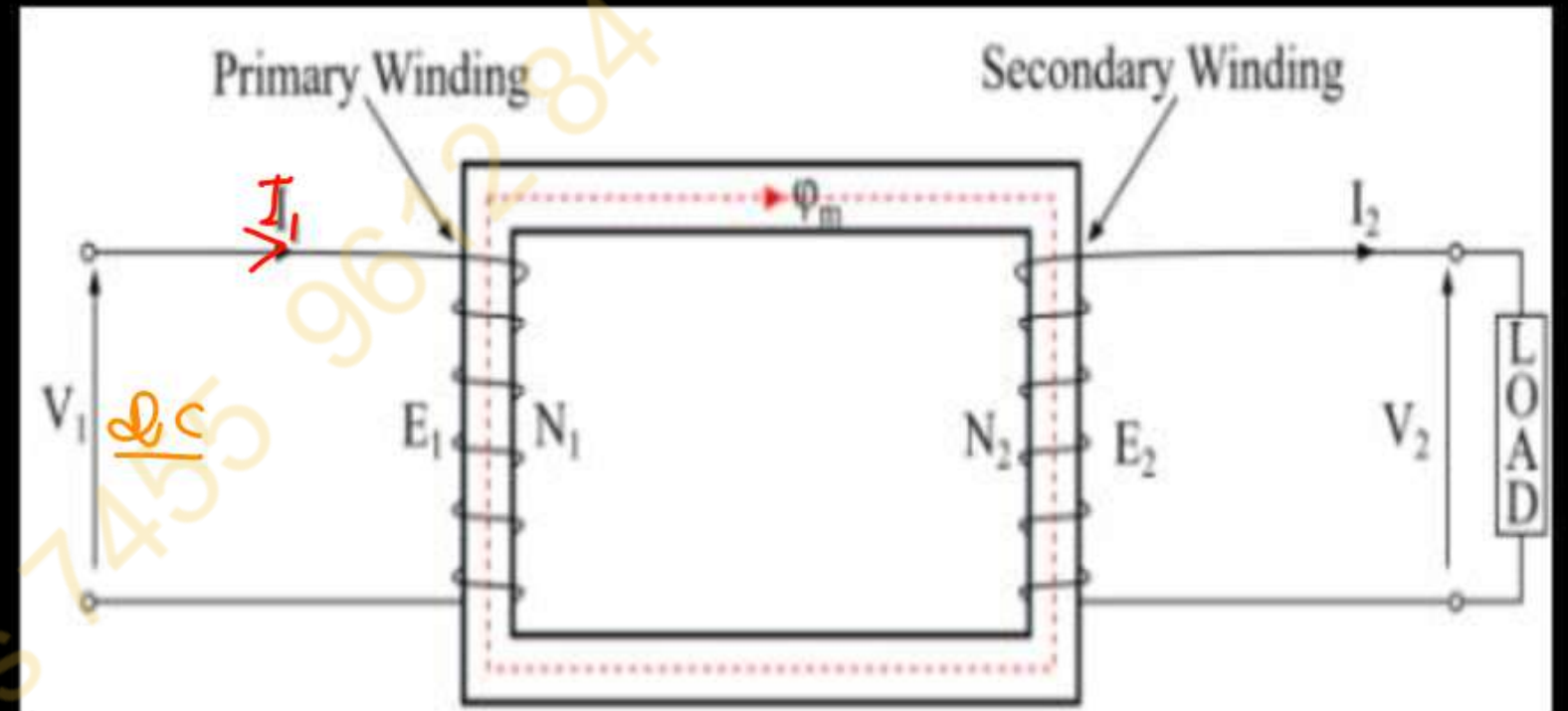
$$K = \frac{V_2}{V_1} = \frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2}$$



Can Transformer work on DC

No

Transformers can be classified on different basis, like types of construction, types of cooling etc.

On the basis of construction

- Core type
- Shell type

On the basis of their purpose

- Step up transformer ($V_2 > V_1$, $N_2 > N_1$)
- Step down " ($V_2 < V_1$, $N_2 < N_1$)

On the basis of type of supply

- 1- ϕ supply
- 3- ϕ supply



Cooling Based

- ① Air Cooled transformer.
- ② Oil Cooled transformer.

Classification of Transformer based on Construction

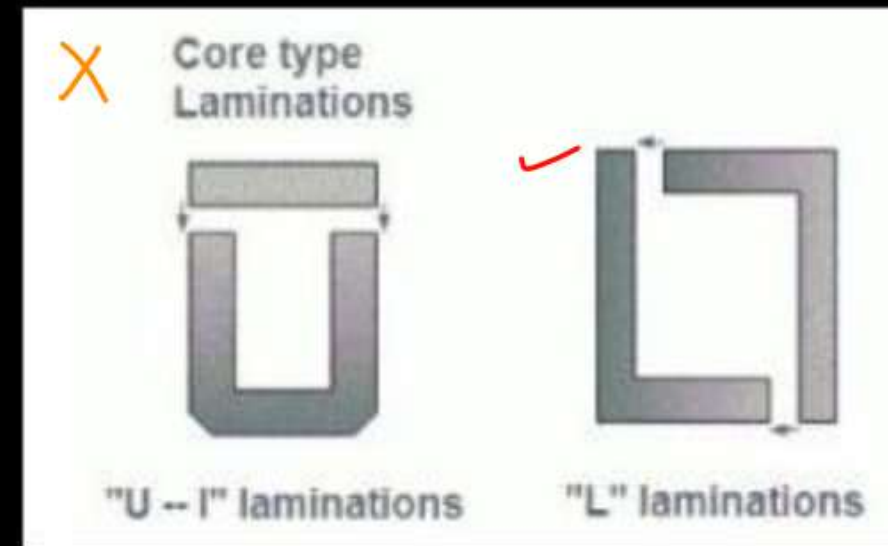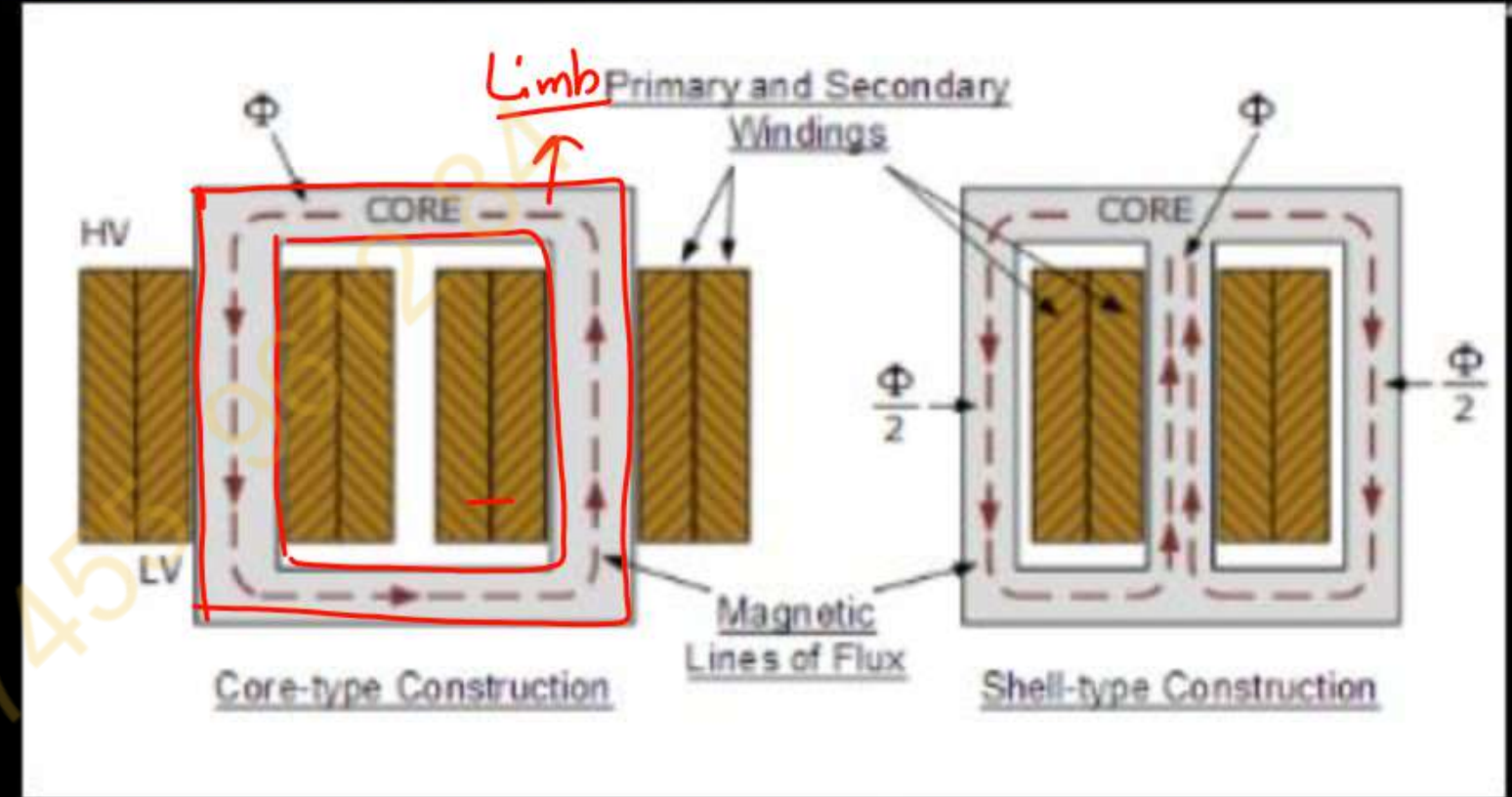- 1. Core type transformer: $\rightarrow$ Winding Surrounds a Considerable part of core.
- 2. Shell-type transformer:

Core Surrounds a Considerable part of the Winding.



M. Imp

$$\phi = \phi_m \sin \omega t$$

Induced E.m.f in primary wdg

$$E_1 = -N_1 \frac{d\phi}{dt}$$

$$E_1 = -N_1 \frac{d}{dt} (\phi_m \sin \omega t)$$

$$= -N_1 \phi_m \cos \omega t \cdot \omega$$

$$= -N_1 \phi_m \omega (\cos \omega t)$$

$$E_1 = +N_1 \phi_m \omega \sin(\omega t - \frac{\pi}{2})$$

$$E_1 = E_{m1} \sin(\omega t - \frac{\pi}{2})$$

E.M.F. Equation of Transformer

$$E_{m1} = N_1 \phi_m \omega$$

$$E_1 = \frac{E_m}{\sqrt{2}} = \frac{N_1 \phi_m 2\pi f}{\sqrt{2}}$$

$$E_1 = 4.44 N_1 \phi_m f$$

Similarly

$$E_2 = 4.44 N_2 \phi_m f$$

Proved

Rating of Transformer

$$\text{Iron loss} \propto V$$

→ depends on voltage

$$\text{Total loss} \propto V, I$$

$$\text{Copper loss} \propto I^2 R$$

$$\propto I^2$$

→ depends on current



Rating KVA

← does not depend on phase angle.

Ideal Transformer on no load

No Losses $R=0$
(2-10% of f.l. current)

- The primary draws a very small current I_1 which is just necessary to produce flux in the core. As it is magnetizing the core, it is called **magnetizing current denoted as I_m** .
- As the transformer is ideal, the winding ~~resistance~~ resistance is zero and it is purely inductive in nature.
- The magnetizing current is very small and lags V_1 by 90° as the winding is purely inductive. This I_m produces an alternating flux Φ which is in phase with I_m .
- The flux links with both the winding producing the induced emf E_1 and E_2 , in the primary and secondary windings respectively.
- According to Lenz's law, the induced emf opposes the cause producing it which is supply voltage V_1 . Hence E_1 is in antiphase with V_1 but equal in magnitude.
- The induced emf E_2 also opposes V_1 hence in antiphase with V_1 but its magnitude depends on N_2 . Thus E_1 and E_2 are in phase.

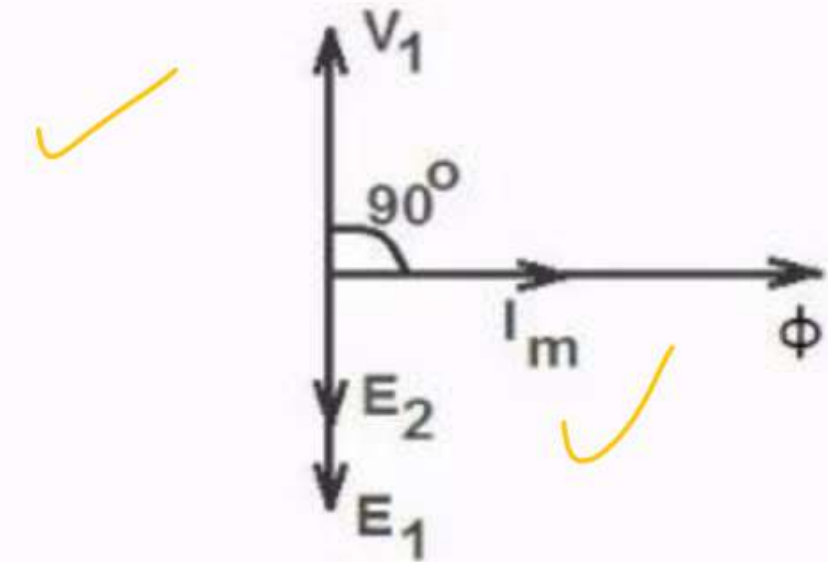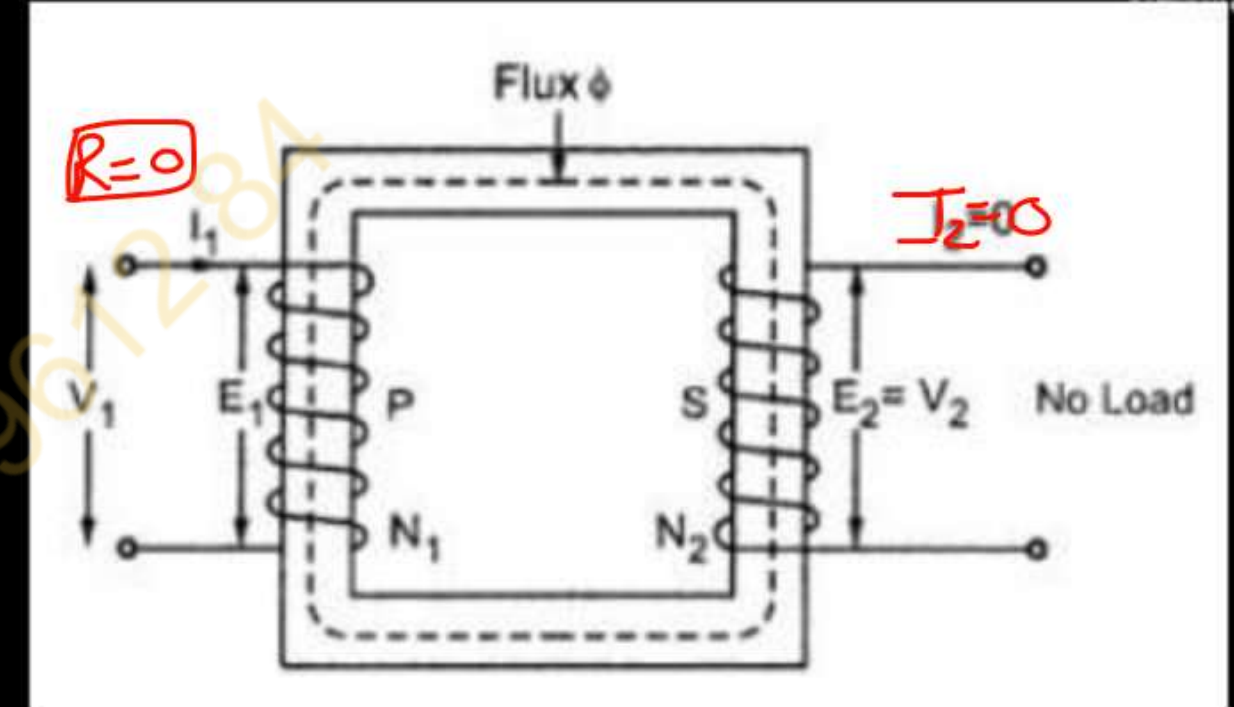

Phasor diagram of an ideal transformer



Practical Transformer on no load

The no-load current consists of two components:

Reactive or magnetizing component I_m :- It produces flux in the core

Active or power component I_w :- It supplies small amount of primary copper loss.

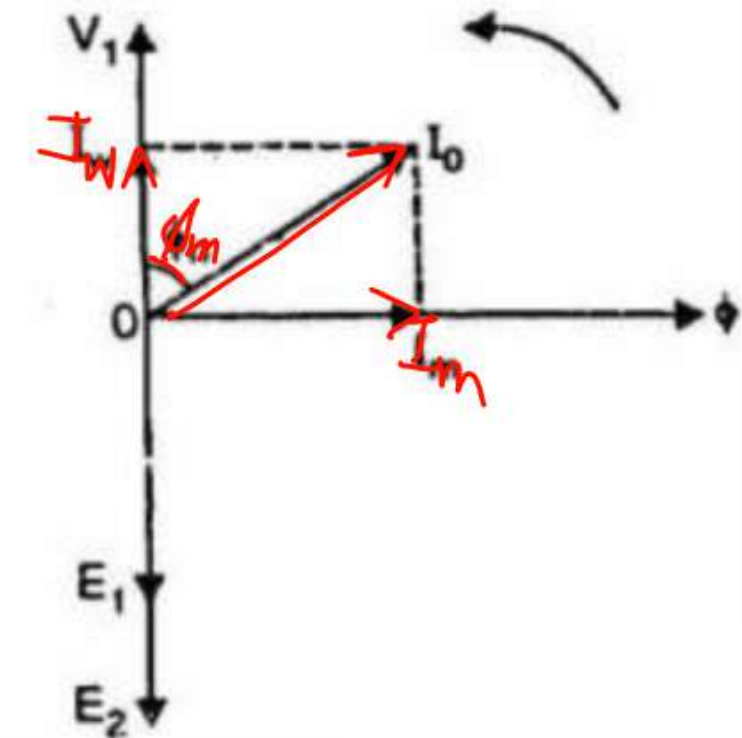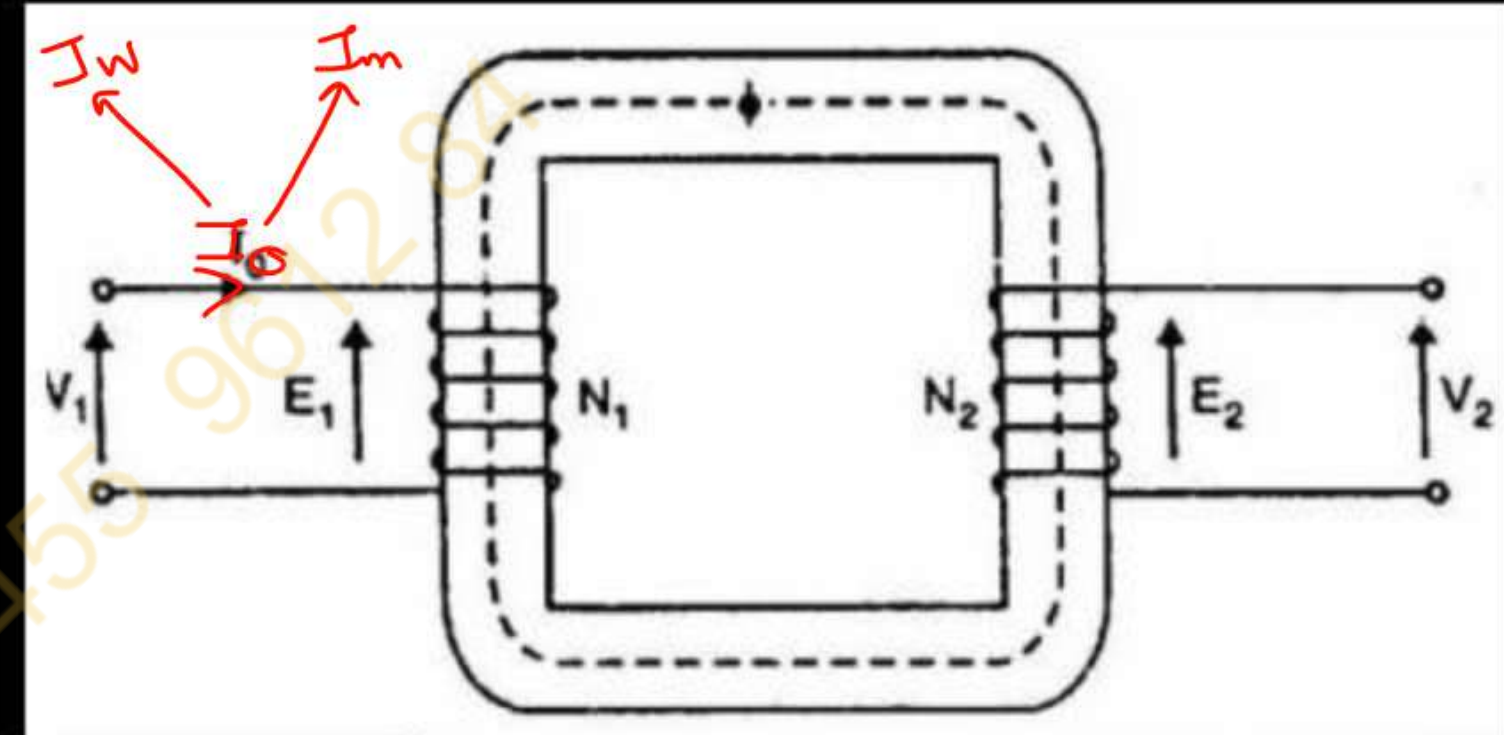Hence the primary no load current I_0 is not 90° behind the applied voltage V_1 but lags it by an angle $\phi_0 < 90^\circ$ as shown in the phasor diagram.



Working component $I_w = I_0 \cos \phi_0$ ✓

No load current $I_0 = \sqrt{I_w^2 + I_m^2}$ ✓

Magnetizing component $I_m = I_0 \sin \phi_0$ ✓

Power factor $\cos \phi_0 = \frac{I_w}{I_0}$ ✓

No load power input $P_0 = V_1 I_0 \cos \phi_0$

Practical Transformer on no load

V_1 V_2

Ex.1 A 25 KVA , 3300/ 230V , 50 Hz , 1 phase transformer draws no load current of 15 A when excited on ~~low~~ ^{low} voltage side and consumes 350 watts. Calculate two components of current . Aktu – 2003-04

Solⁿ 25 KVA, $V_2 = 230$, $V_1 = 3300$, $f = 50$ Hz , $I_0 = 15$ A

$$P = 350 \text{ watt}$$

$$I_w = I_0 \cos \phi_0 \quad , \quad I_m = I_0 \sin \phi_0$$

$$P = V_2 I_0 \cos \phi_0$$

$$350 = 230 \times 15 \cos \phi_0$$

$$\cos \phi_0 = \frac{350}{230 \times 15}$$

$$= 0.10$$

$$\phi_0 = 84.1^\circ$$

$$I_w = 15 \times 0.10$$

$$= 1.5 \text{ Amp}$$


$$I_m = 15 \times \sin 84.1^\circ$$

$$= 14.92 \text{ Amp}$$

Ans.

Transformer on Load

- When the secondary is kept open, it draws the no-load current from the main supply. The no-load current induces the mmf $N_0 I_0$ and this force set up the flux Φ in the
- When the load is connected to the secondary of the transformer, I_2 current flows through their secondary winding. The secondary current induces the mmf $N_2 I_2$ on the secondary winding of the transformer. This force set up the flux ϕ_2 in the transformer core. The flux ϕ_2 opposes the flux ϕ , according to **Lenz's law**.

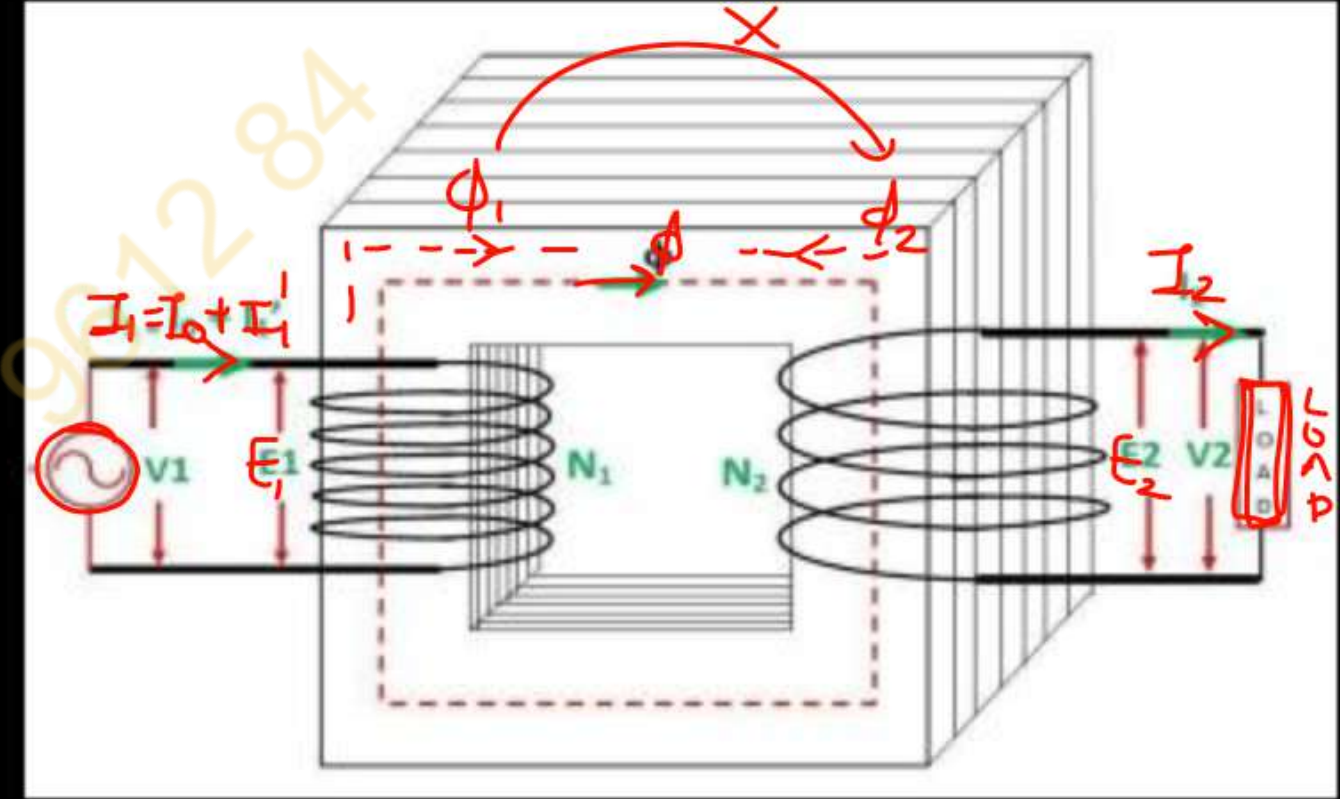

- flux ϕ_2 opposes the flux ϕ , the resultant flux of the transformer decreases and this flux reduces the induced EMF E_1 . Thus, the strength of V_1 is more than E_1 and an additional primary current I_1' drawn from the mains.
- The additional current is used for restoring the original value of the flux in the core of the transformer so that $V_1 = E_1$. The primary current I_1' is in phase opposition with the secondary current I_2 .
- The additional current I_1' induces the mmf $N_1 I_1'$. And this force set up the flux ϕ'_1 . The direction of the flux is the same as that of the ϕ and it cancels the flux ϕ_2 which induces because of the MMF $N_2 I_2$

Transformer on Load

- Now, $N_1 I_1' = N_2 I_2$
Therefore,


$$I_1' = \left(\frac{N_2}{N_1} \right) I_2 = K I_2$$

$$\frac{I_1'}{I_2} = \frac{N_2}{N_1}$$

$$I_1' = \left(\frac{N_2}{N_1} \right) I_2 = K I_2$$

- The phase difference between V_1 and I_1 gives the power factor angle ϕ_1 of the primary side of the transformer.
- The power factor of the secondary side depends upon the type of load connected to the transformer.
- The total primary current I_1 is the vector sum of the currents I_0 and I_1' .

$$\bar{I}_1 = \bar{I}_0 + \bar{I}_1'$$

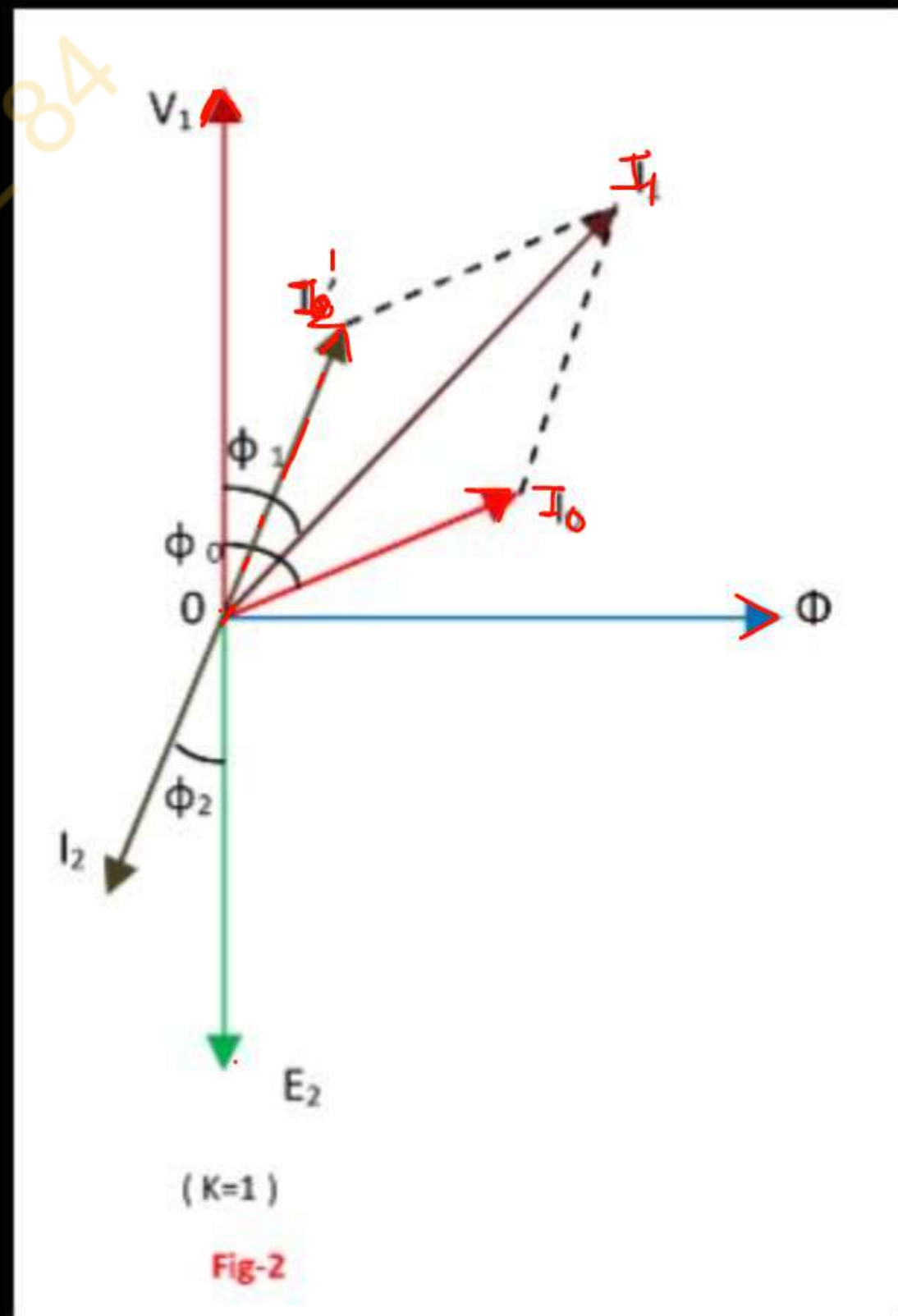

Transformers

Unit-3 | Lec-3

Today's Target

- ✓ Equivalent Circuit of Transformer *7 marks*
- ✓ Efficiency of transformer *7 marks*
- ✓ Voltage Regulation

Equivalent circuit of Transformer


Concept of Leakage reactance:-

→ leakage Reactance

→ Resistive drop

$$X_{01} \Rightarrow X_1 + \frac{X_2}{k^2}$$
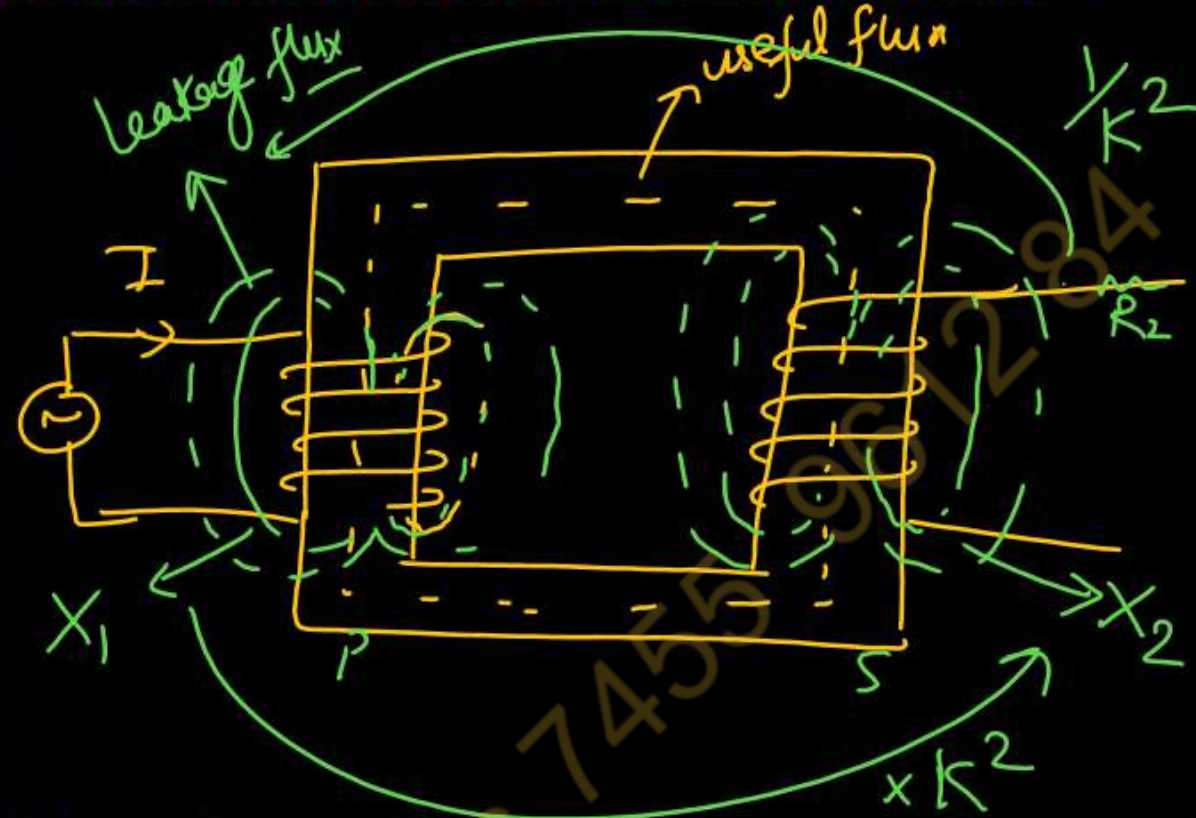
$$R_{01} \Rightarrow R_1 + \frac{R_2}{k^2}$$



$$R_{02} \Rightarrow R_2 + R_1 k^2$$

$$X_{02} \Rightarrow X_2 + X_1 k^2$$

Concept of equivalent resistance:- referred to primary and secondary


$$\begin{aligned} \checkmark \text{ Total losses} &= I_1^2 R_1 + I_2^2 R_2 \\ \cancel{I_1^2} R_{01} &= \cancel{I_1^2} \left(R_1 + \left(\frac{I_2}{I_1} \right)^2 R_2 \right) \\ R_{01} &= R_1 + \left(\frac{I_2}{I_1} \right)^2 R_2 = R_1 + \frac{R_2}{k^2} \end{aligned}$$

$$\cancel{\frac{I_2^2}{I_2}} R_{02} = \cancel{\frac{I_2^2}{I_2}} \left(\left(\frac{I_1}{I_2} \right)^2 R_1 + R_2 \right)$$


$$R_{02} = k^2 R_1 + R_2$$

Equivalent circuit of Transformer

Exact Equivalent circuit.

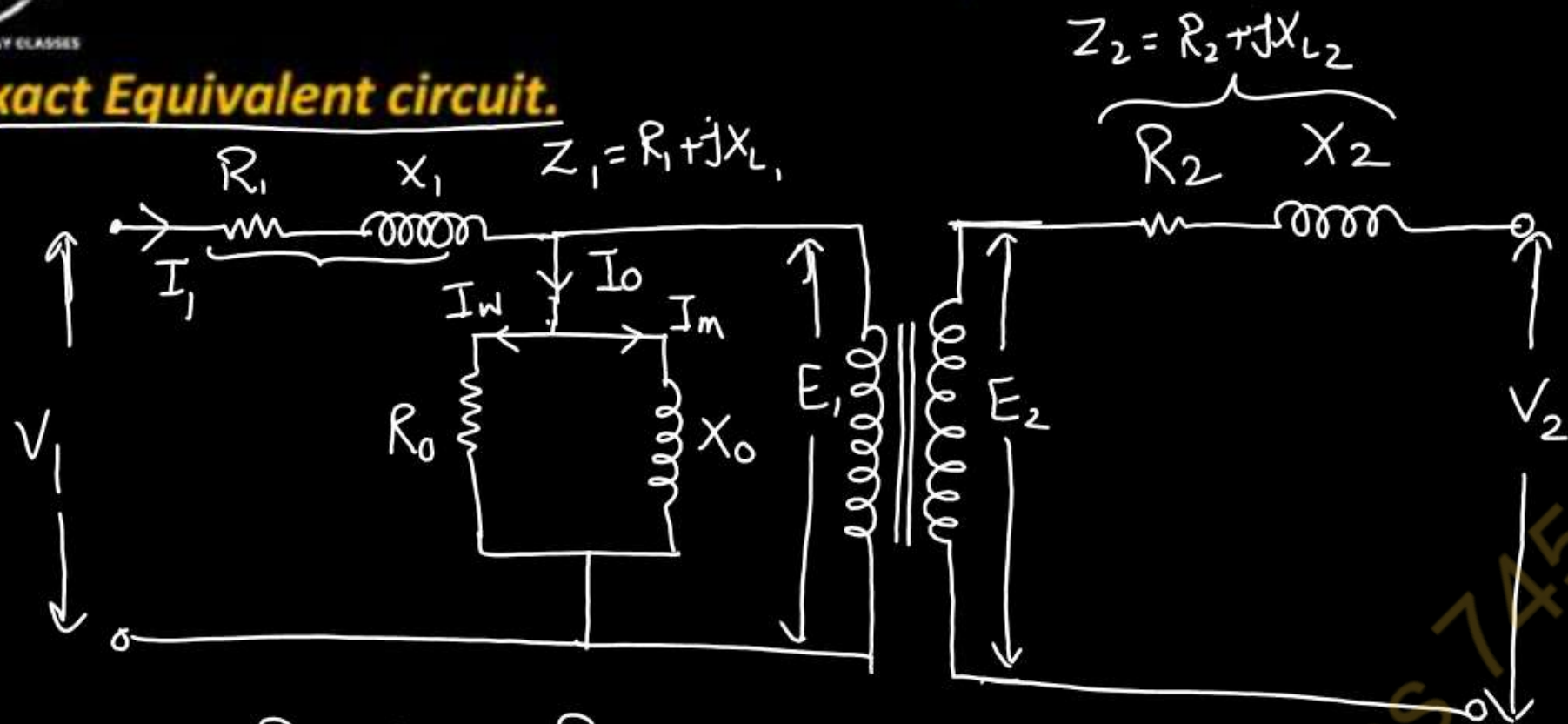


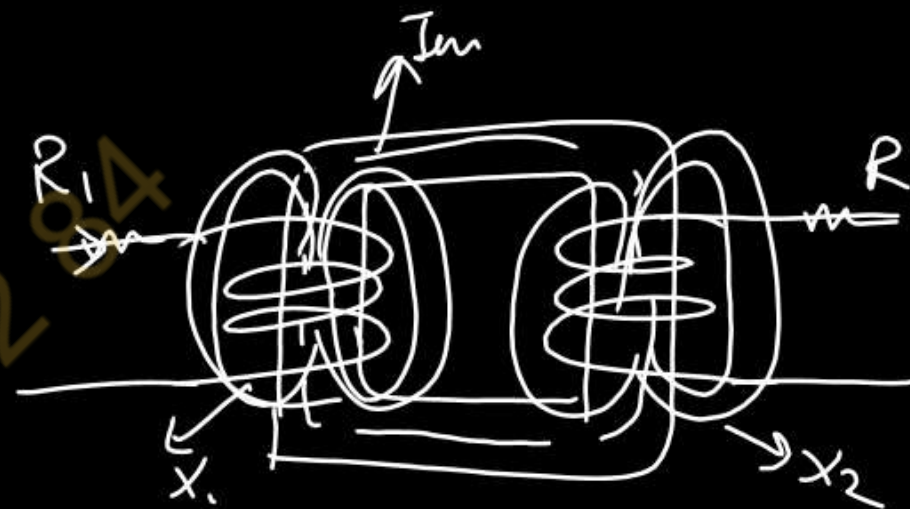R_1, R_2 = Primary & Secondary resistance of winding
 X_1, X_2 = " " leakage reactance "
 R_0, X_0 = No load Component
 E_1, E_2 = " induced e.m.f.



01

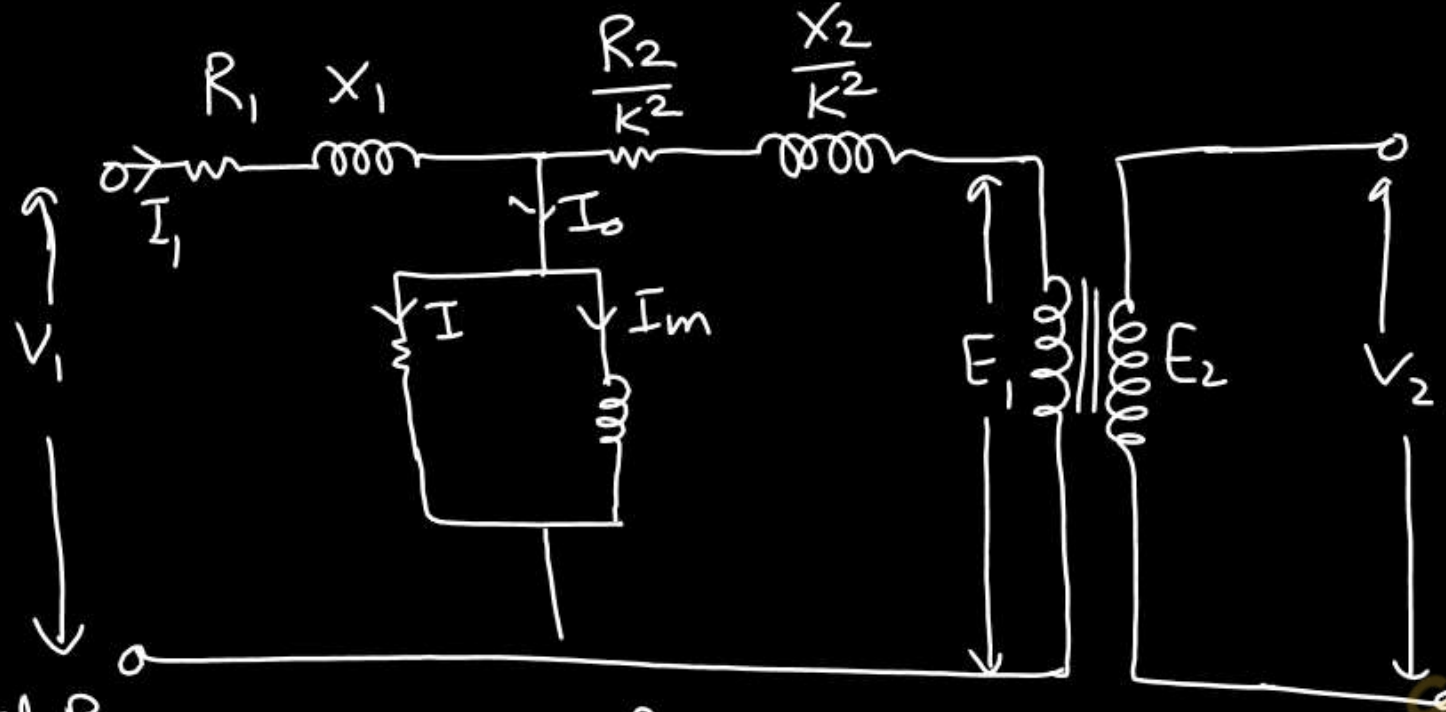Exact Equivalent circuit referred to Primary




Total Res
reff to Primary $R_{01} = R_1 + \frac{R_2}{k^2}$, $X_{01} = X_1 + \frac{X_2}{k^2}$

Total Imp reff to
Primary $Z_{01} = R_{01} + jX_{01}$

Gateway classes 7455 961284

Equivalent circuit of Transformer

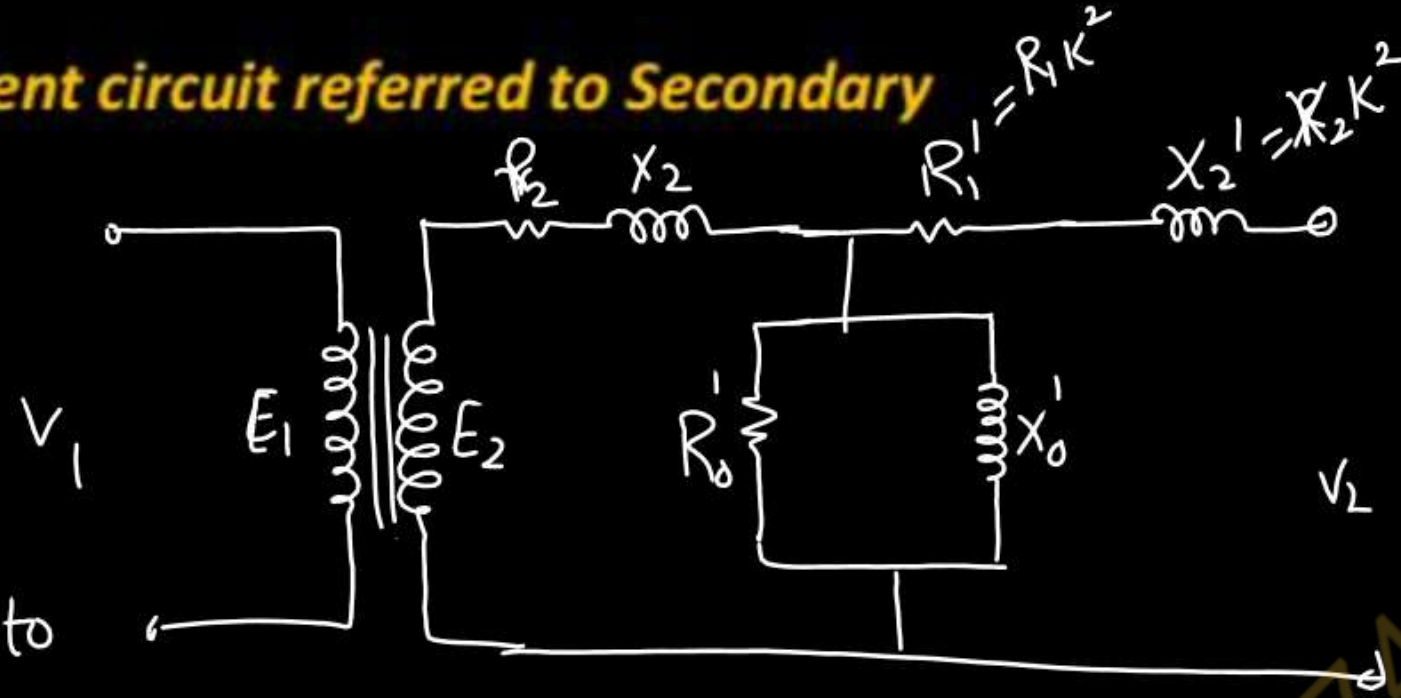Exact Equivalent circuit referred to Secondary



Total Res. R_{eff} to


$$\text{Secondary } R_{02} = R_2 + R_1 K^2$$

$$X_{02} = X_2 + X_1 K^2$$


$$Z_{02} = R_{02} + jX_{02}$$

Approximate Equivalent circuit

Ref to Secondary

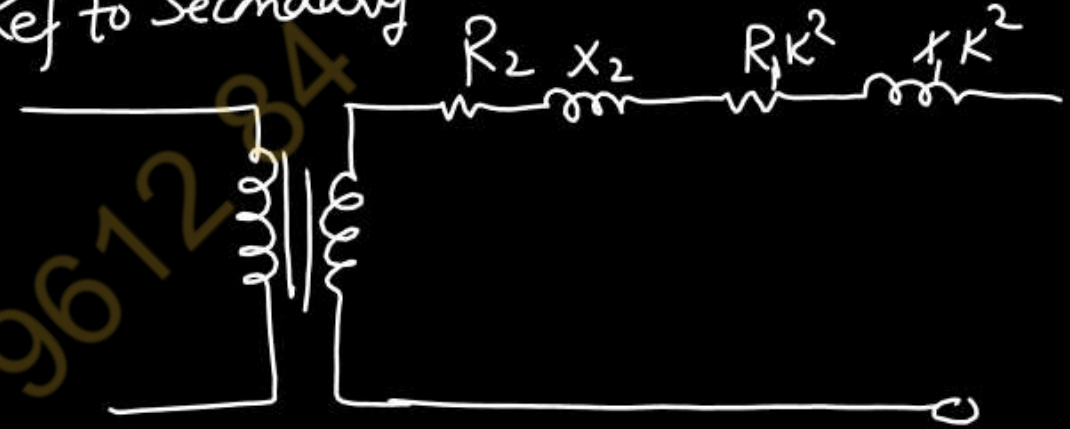

Ref to Primary

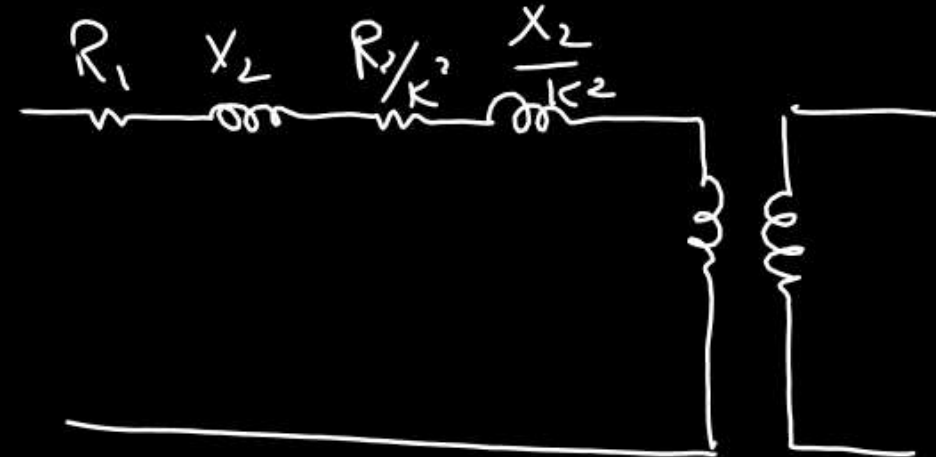


Losses in a Transformer

• Core Loss/ Iron Loss/ Fixed Loss/ Constant Loss

- **Hysteresis Loss:-** When a magnetic material is subjected to cycle of magnetization, a power loss occurs due to molecular friction in the material. Therefore, energy is required in the material to overcome this opposition. This loss being in the form of heat and is termed as *hysteresis loss*.


$$\text{Area of hysteresis loop} \propto B_{\max}^{1.6}$$
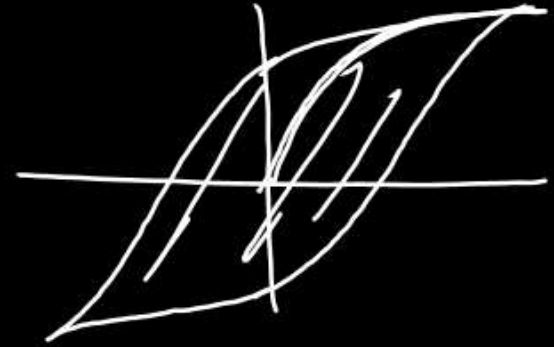
$$\text{Hysteresis power loss, } P_h = \eta B_{\max}^{1.6} f V \text{ Watts}$$



- **Eddy Current Loss:-** When a magnetic material is subjected to a changing magnetic field, a voltage is induced in the material according to Faraday's law of electromagnetic induction. Since the material is conducting, the induced voltage circulates currents within the body of the magnetic material. These circulating currents are known as *eddy currents*. These eddy currents cause I^2R loss in the material, known as *eddy current loss*.
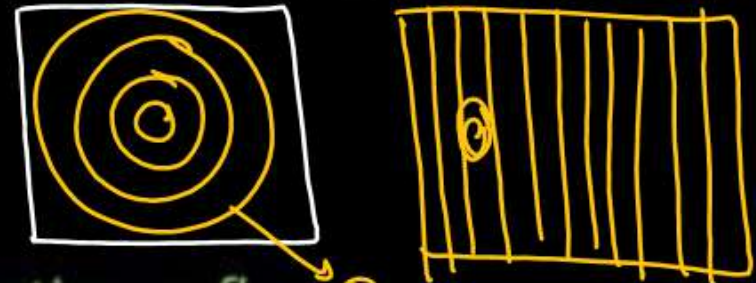
$$\text{Eddy current power loss, } P_e = K_e B_{\max}^2 f^2 t^2 V \text{ Watts}$$



Where K_e = Eddy current coefficient, $B_{\max}$ = Maximum flux density, f = frequency of magnetization or flux, t = thickness of lamination, and V = Volume of magnetic material.

Eddy Current

Copper Loss/ Variable Loss/ I^2R Loss

- **Copper Loss:-** The losses are occurs due the resistance of primary and secondary winding. These losses are depends upon the magnitude of current in winding.

$$P_{cu} \propto I^2$$
$$P_{cu} = I^2 R$$

- Thus for a Transformer Total Losses = Iron Loss + Copper Loss = $P_i + P_{cu}$

Methods of reducing Losses in a Transformer


Iron Loss:- (i) Choice of Material for Iron Core (steel of high silicon content)

(ii) Use of Thin Laminated Core

Copper Loss/ Variable Loss/ I^2R Loss

(i) Reduce resistance of winding (use of thick wire)

• Efficiency of Transformer:-

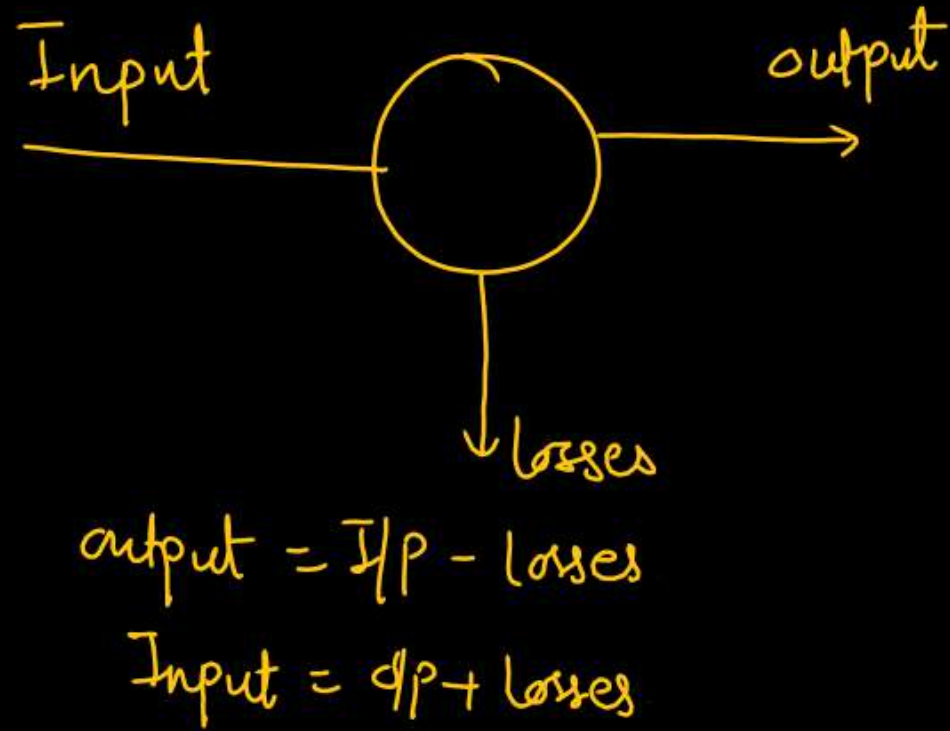

Efficiency of Transformer

Efficiency

$$\% \eta = \frac{\text{output}}{\text{Input}} \times 100$$

$$\% \eta_{fl} = \frac{V_2 I_2 \cos \phi}{V_2 I_2 \cos \phi + P_i + P_{cu}} \times 100$$

at any load

$$\% \eta = \frac{x V_2 I_2 \cos \phi}{x V_2 I_2 \cos \phi + P_i + x^2 P_{cu}}$$

x = load factor
half load $x = \frac{1}{2}$

Efficiency of Transformer

Condition of Maximum Efficiency of a Transformer:-

$$\eta = \frac{V_2 I_2 \cos \phi}{V_2 I_2 \cos \phi + P_{l0} + I_2^2 R_{02}}$$

$$\frac{d\eta}{dI_2} = 0$$

$$\frac{(V_2 I_2 \cos \phi + P_{l0} + I_2^2 R_{02})(V_2 \cos \phi) - (V_2 I_2 \cos \phi)(V_2 \cos \phi + 0 + 2I_2 R_{02})}{(V_2 I_2 \cos \phi + P_{l0} + P_{cu})^2} = 0$$

$$(V_2 I_2 \cos \phi + P_{l0} + P_{cu}) \cancel{V_2 \cos \phi} = \cancel{V_2 I_2 \cos \phi} (V_2 \cos \phi + 2I_2 R_{02})$$

$$\cancel{V_2 I_2 \cos \phi} + P_{l0} + P_{cu} = \cancel{V_2 I_2 \cos \phi} + \underbrace{2I_2^2 R_{02}}_{P_{cu}}$$

$$P_{l0} = I_2^2 R_{02}$$

$$P_{l0} = P_{cu}$$

At any Load

$$P_{l0} = x^2 P_{cu}$$

Efficiency of Transformer

Load Current at Maximum Efficiency :-

$$P_i = P_{cu}$$

$$P_i = I_2^2 R_{02}$$

$$I_2^2 = \frac{P_i}{R_{02}}$$

$$\frac{I_2}{I_{fL}} = \sqrt{\frac{P_i}{P_{cu fL}}}$$

$$\frac{I_2}{I_{fL}} = \sqrt{\frac{P_i}{I_{fL}^2 R_{02}}}$$

$$I_{2m} = I_{fL} \sqrt{\frac{P_i}{P_{cu fL}}}$$

KVA at Maximum Efficiency:-

$$(KVA)_{\eta_{max}} = V_2 I_{2m} \eta = V_2 I_{fL} \sqrt{\frac{P_i}{P_{cu}}} \eta = (KVA)_{fL} \sqrt{\frac{P_v}{P_{cu}}}$$

Gateway classes 7455 9612 84

Voltage Regulation of a Transformer

$$\therefore \text{Voltage Regulation} = \frac{E_2 - V_2}{V_2}$$

$$= \frac{(I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi)}{V_2}$$

+ Lagging

- Leading

Gateway classes 7455 9612 84

AKTU : FUNDAMENTALS OF ELECTRICAL ENGINEERING

Transformers

Unit-3 Lec-4

Today's Target

- ✓ PYQ On Equivalent Circuit of Transformer ✓
- ✓ PYQ On Efficiency of Transformer ✓
- ✓ PYQ On Voltage regulation of Transformer

Ex-1 A 20kVA, 2000V/200V, single-phase, 50 Hz transformer has a primary resistance of 1.5Ω and reactance of 2Ω . The secondary resistance and reactance are 0.015Ω and 0.02Ω respectively. The no load current of transformer is 1A at 0.2 power factor. Determine: (i) Equivalent resistance, reactance and impedance referred to primary (ii) Supply current (iii) Total copper loss Draw approximate equivalent circuit **2021-22**

$$P = 20 \text{ kVA}$$

$$V_1 = 2000, V_2 = 200$$

$$K = \frac{200}{2000} = \frac{1}{10}$$

Referred to Primary

$$R'_1 = \frac{R_2}{K^2} = \frac{0.015}{\left(\frac{1}{10}\right)^2} = 1.5 \Omega$$

$$X'_1 = \frac{X_2}{K^2} = \frac{0.02}{\left(\frac{1}{10}\right)^2} = 2 \Omega$$

Total Resistance on primary side

$$R_{01} = R_1 + R'_1 = 1.5 + 1.5 = 3 \Omega$$

Similarly

$$X_{01} = X_1 + X'_1 = 2 + 2 = 4 \Omega$$


$$Z_{01} = R_{01} + jX_{01} = (3 + 4j)$$

$$(i) I = \frac{P}{V} = \frac{20 \times 10^3}{2000} = 10 \text{ A}$$

(ii) Total Copper loss

$$P_{cu} = I_1^2 R_{01} = 10^2 \times 3 = 300 \text{ watt}$$

Ans

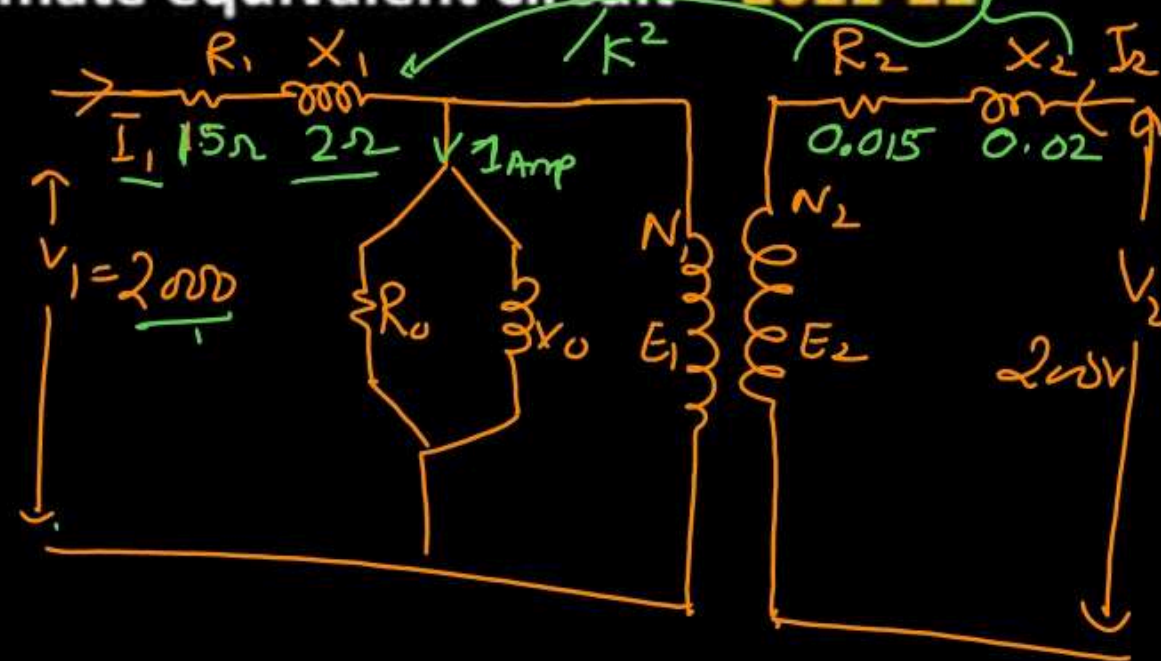

Ex-2 An $1100/110V$, $22KVA$, 1ϕ transformer has primary resistance and reactance 4Ω and 6Ω respectively. The secondary resistance and reactance are 0.04Ω and 0.065Ω respectively. Calculate (i) Equivalent resistance and reactance of secondary referred to primary. (ii) Total resistance & reactance referred to ~~primary~~ ^{secondary}. (iii) ~~Equivalent resistance and reactance of primary referred to secondary~~. (iv) Total copper loss

$$R_1 = 4\Omega, X_1 = 6\Omega$$

$$R_2 = 0.04\Omega, X_2 = 0.065\Omega$$

(i) Referred to Primary

$$R_{01} = R_1 + \frac{R_2}{K^2} = 4 + \frac{0.04}{(\frac{1}{10})^2} = 8\Omega$$

$$X_{01} = X_1 + \frac{X_2}{K^2} = 6 + \frac{0.065}{(\frac{1}{10})^2} = 12.5\Omega$$

$$K = \frac{V_2}{V_1} = \frac{1}{10}$$

(ii) Referred to Secondary

$$R_{02} = R_2 + R_1 K^2 = 0.04 + 4 \times \frac{1}{100} = 0.08\Omega$$

$$X_{02} = X_2 + X_1 K^2 = 0.065 + 6 \times \frac{1}{100} = 0.125\Omega$$

Total Copper loss

$$P_{Cu} = I_1^2 R_{01} = I_2^2 R_{02}$$

$$P_{Cu} = 20^2 \times 8 = (200)^2 \times 0.08$$

$$P_{Cu} = 3200W = 3200W$$

$$I_1 = \frac{P}{V_1} = \frac{22 \times 10^3}{1100}, I_2 = \frac{P}{V_2} = \frac{22000}{110}$$

$$I_1 = 20A$$

$$I_2 = 200A$$

$$P_{Cu} = I_1^2 R_1 + I_2^2 R_2$$

$$= 20^2 \times 4 + (200)^2 \times 0.04$$

$$= 1600 + 1600$$

$$= 3200W$$

Ex-3 A 40 KVA transformer has iron loss of 450W and full load copper loss of 850W. if the power factor of the load is 0.8 lagging, calculate: (i) Full load efficiency (ii) The load at which the maximum efficiency occurs and (iii) The maximum efficiency. **2021-22**

40 KVA, $P_i = 450$ W, $P_{cu} = 850$ W, $\cos\phi = 0.8$

$$\eta_{fL} = \frac{V_2 I_2 \cos\phi_2}{V_2 I_2 \cos\phi_2 + P_i + P_{cu}} = \frac{40 \times 10^3 \times 0.8}{(40 \times 10^3 \times 0.8) + 450 + 850}$$
$$= 0.96$$

$$\therefore \eta_{fL} = 96\%$$

$$KVA_{\eta_{max}} = KVA_{fL} \times \sqrt{\frac{P_i}{P_{cu}}} = 40 \times 10^3 \times \sqrt{\frac{450}{850}}$$
$$= 29104.27 \text{ VA}$$

$$\eta_{max} = \frac{29104.27 \times 0.8}{29104.27 \times 0.8 + 2P_i} \times 100$$
$$= 96.27\%$$

$$P_i = P_{cu}$$

Ex-4 A single phase 100KVA 6.6kv , 230V 50Hz transformer has 90% efficiency at 0.8 lagging power factor both at full load and also at half load. Determine iron and copper loss at full load for the transformer. **2019-20**

$$\% \eta_{f.l} = 90 = \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + P_{i^0} + P_{cu}} \times 100$$

$$0.9 = \frac{100 \times 10^3 \times 0.8}{100 \times 10^3 \times 0.8 + (P_{i^0} + P_{cu})}$$

$$[80000 + (P_{i^0} + P_{cu})] 0.9 = 80000$$

$$0.9(P_{i^0} + P_{cu}) = 80000 - 72000 = 8000$$

$$P_{i^0} + P_{cu} = \frac{8000}{0.9} = 8888.9 \text{ W} \quad (1)$$

$$\eta_{H.L} = 0.9 = \frac{x V_2 I_2 \cos \phi_2}{x V_2 I_2 \cos \phi_2 + P_{i^0} + x^2 P_{cu}}$$

$$0.9 = \frac{50000 \times 0.8}{50000 + P_{i^0} + \frac{P_{cu}}{4}}$$

$$36000 + 0.9(P_{i^0} + \frac{P_{cu}}{4}) = 40000$$

$$0.9(P_{i^0} + \frac{P_{cu}}{4}) = 40000 - 36000 = 4000$$

$$P_{i^0} + \frac{P_{cu}}{4} = 4444.5 \quad (2)$$

$$x = \frac{1}{2}$$

Solve Eqs (1) & (2)

$$P_{i^0} = 2962.96 \text{ W}$$

$$P_{cu} = 5925.92 \text{ W} \quad \underline{\underline{Ans}}$$

Ex-5 The maximum efficiency of a 100 KVA, 1100/440 V, 50 Hz transformer is 96%, This occurs at 75% of full load at 0.8 p.f. lagging. Find the efficiency of transformer at 3.4 FL at 0.6 p.f. leading. **2018-19**

$$\eta_{max} = 0.96 = \frac{0.75 \times 100 \times 10^3 \times 0.8}{75000 \times 0.8 + 2P_{i0}}$$

$$x = 0.75$$

$$57600 + 1.92P_{i0} = 60000$$

$$P_{i0} = 1250 \text{ watt}$$

at max η .

$$P_{i0} = x^2 P_{cu}$$

$$P_{cu} = \frac{P_{i0}}{x^2} = \frac{1250}{(0.75)^2}$$

$$P_{cu} = 2222.22 \text{ watt}$$

$$x = 3.4$$

$$\eta = \frac{x V_2 I_2 \cos \phi}{x V_2 I_2 \cos \phi + P_{i0} + P_{cu} x^2}$$

$$= \frac{3.4 \times 100 \times 10^3 \times 0.6}{3.4 \times 100 \times 10^3 \times 0.6 + 1250 + 2222.22 \times (3.4)^2}$$

$$= \frac{204000}{204000 + 1250 + 25777.78} = 88.33\%$$

$$\eta_{3.4} = 88.33\%$$

Ex-6 In a 50 KVA , $1100/220 \text{ V}$ transformer, the iron and copper losses at full load are 350 W and 425 W respectively. Calculate the efficiency at (i) full load and half load unity power factor (ii) full load 0.8 Power factor (iii) maximum efficiency and load at which maximum efficiency occurs assuming the load to be resistive. **2018-19**

$\cos \phi = 1$

$1 \rightarrow 0.8$

$$\eta_{fL} = \frac{50 \times 10^3 \times 1}{50 \times 10^3 \times 1 + 350 + 425}$$

$$= 0.9847$$

$$\eta_{fL} = 98.47\%$$

at half load $x = \frac{1}{2}$, kVA

$$\eta_{H.L} = \frac{\frac{1}{2} \times 50 \times 10^3 \times 1}{\frac{1}{2} \times 50 \times 10^3 \times 1 + 350 + 425 \times \left(\frac{1}{2}\right)^2}$$

$$\eta_{H.L} = 98.20\%$$

$\cos \phi = 0.8$

$$KVA_{max} = KVA_{fl} \sqrt{\frac{P_i}{P_{cu}}}$$

$$= 50 \times 10^3 \times \sqrt{\frac{350}{425}}$$

$$= 45374.26 \text{ VA}$$

$$\eta_{max} = \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + 2 P_{i0}}$$

$$= \frac{45374.26 \times 1}{45374.26 \times 1 + 2 \times 350}$$

$$\eta_{max} = 98.48\%$$


$\cos \phi = 1$

Solved
Ex-7 A 4kVA, 200/400 V, 50 Hz, single phase transformer has equivalent resistance referred to primary as 0.15Ω . Calculate, (i) The total copper losses on full load (ii) The efficiency while supplying full load at 0.9 power factor lagging (iii) The efficiency while supplying half load at 0.8 power factor leading. Assume total iron losses equal to 60 W **2018-19**

Gateway classes 7455 961234

Ex-8 Calculate the voltage regulation of a transformer in which ohmic drop is 1% and reactance drop is 5% of the voltage at the following power factor (i) 0.8 lagging (ii) 0.8 leading **2005-06**
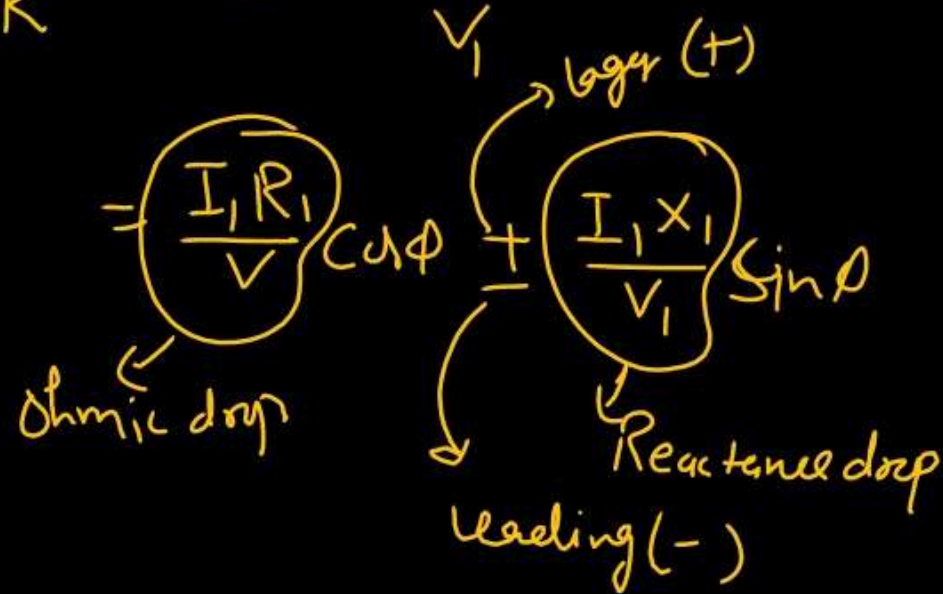
$$V_R = \frac{I_1 R_1 \cos \phi \pm I_1 X_1 \sin \phi}{V_1}$$



(i) $\cos \phi = 0.8$, $\sin \phi = 0.6$

$$V_R = (1 \times 0.8) + (5 \times 0.6)$$

$$= 0.8 + 3$$

$$V_R = 3.8 \%$$

(ii) $V_R = (1 \times 0.8) - (5 \times 0.6)$

$$V_R = -2.2 \%$$

Q.1 A 25kVA, 2000/200V transformer has full load copper and iron losses of 1.8kW and 1.5kW respectively. Calculate efficiency at half the rated kVA and at unity power factor, the efficiency at full load and at 0.8 pf lagging and maximum efficiency. **2020-21**

Q.2 In a 25 KVA, 2000/200 V transformer, the constant and variable losses are 350 W and 400 W respectively. Calculate the efficiency on unity power factor at (i) full load and (ii) half load. **2019-20**

Gateway classes 7455961234

For more Subject/pdf Notes
Download **Gateway Classes** Application
From Google Play store

Link in Description

Thank You

AKTU



B. Tech I-Year

Gateway Classes



Full Courses Available in App

AKTU B.Tech I- Year : All Branches

AKTU B.Tech II- Year

Branches : 1. CS IT & Allied

2. EC & Allied

3. ME & Allied

4. EE & Allied

Downlod App Now



**Full
Courses**

✓ **V. Lectures**

✓ **Pdf Notes**

✓ **AKTU PYQs**

✓ **DPP**